

# Chapter 26: Direct current circuit


- Resistors in circuits
- Equivalent resistance
- The nature of the electric potential and current in circuit
- Kirchhoff's rules (for complicated circuit analysis)

# Resistors in circuit

In circuits, resistors are the locations where **electric potential drops**. → when there is no resistance, there will be no potential drop
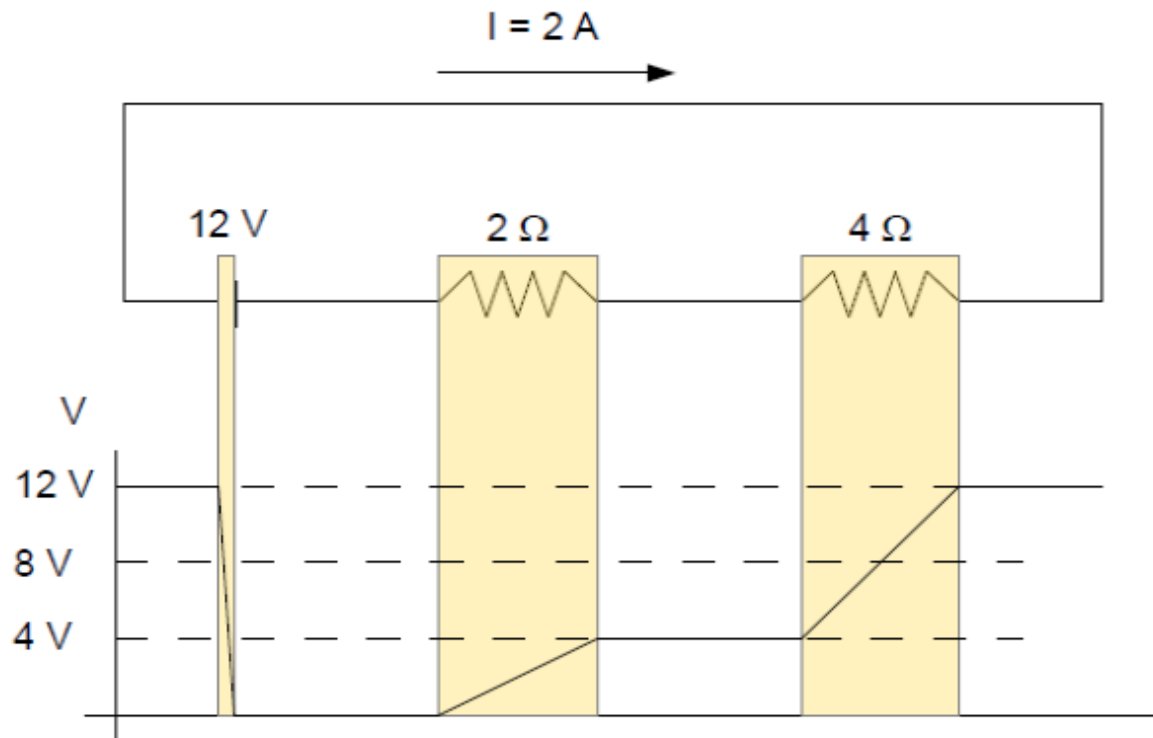
# Resistors in circuit

In circuits, resistors are the locations where **electric potential drops**. → when there is no resistance, there will be no potential drop




# Resistors in circuit

Use Ohm's law for each individual resistors: Each resistor has its own resistance, potential drop and current flow

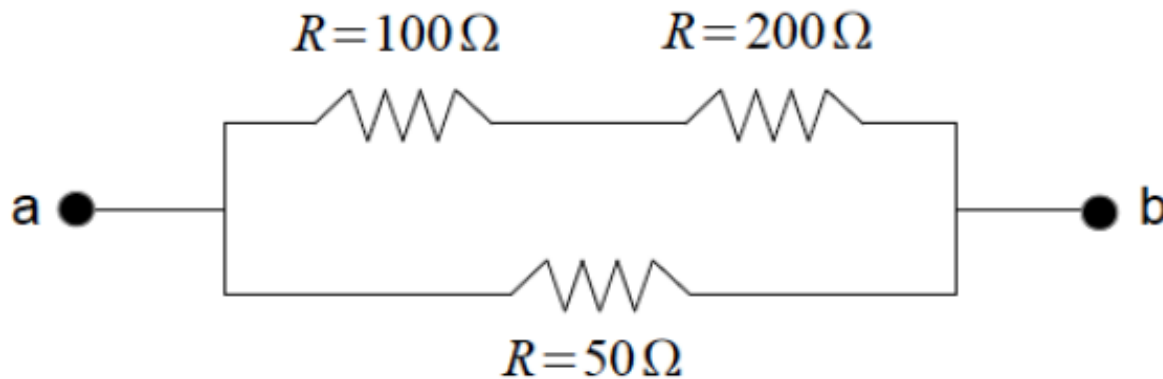
# Resistors in circuit

Use Ohm's law for each individual resistors: Each resistor has it's own resistance, potential drop and current flow



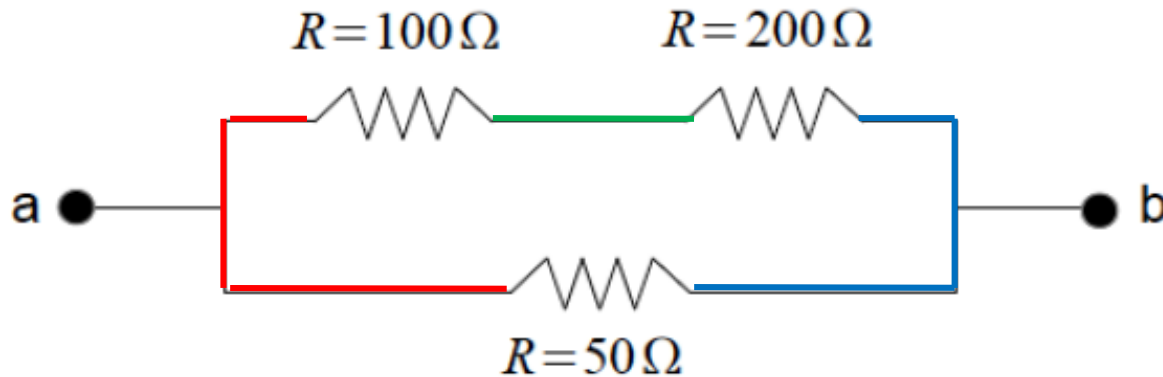
# Resistors in circuit

Use Ohm's law for each individual resistors: Each resistor has it's own resistance, potential drop and current flow



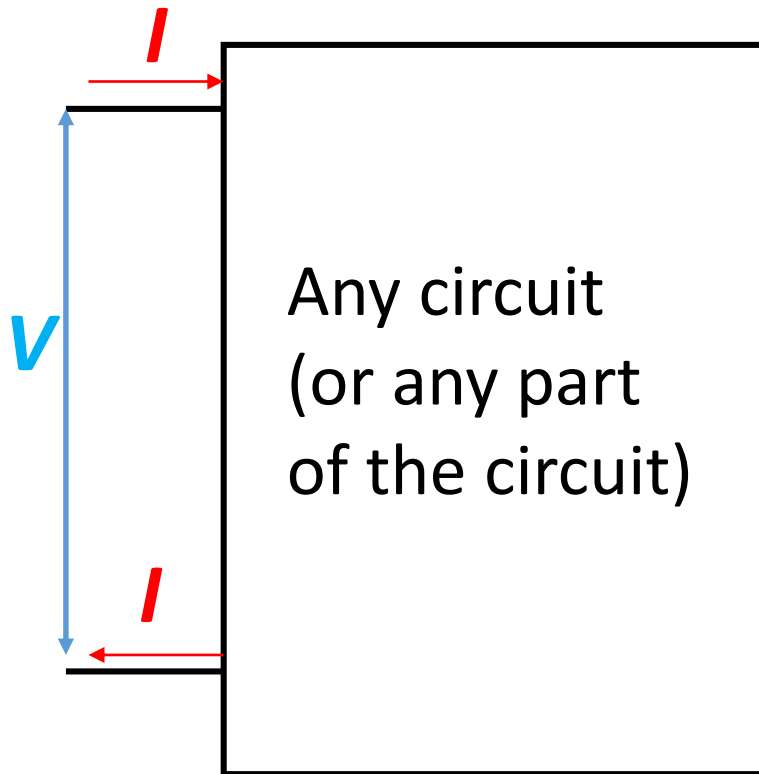
# Equivalent resistance

Equivalent resistance is used to simplify circuit.



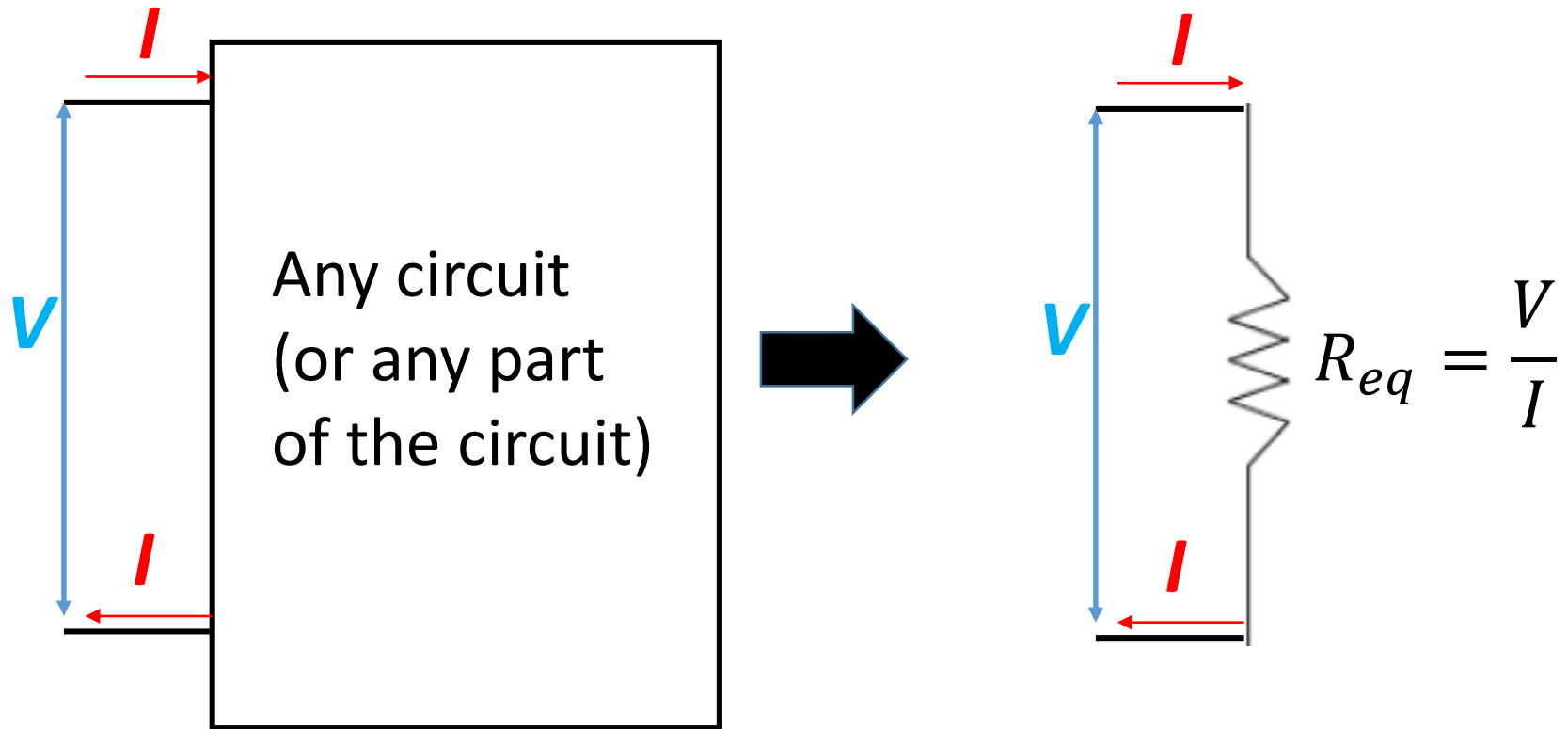
# Equivalent resistance

Equivalent resistance is used to simplify circuit.






# Parallel and series connections

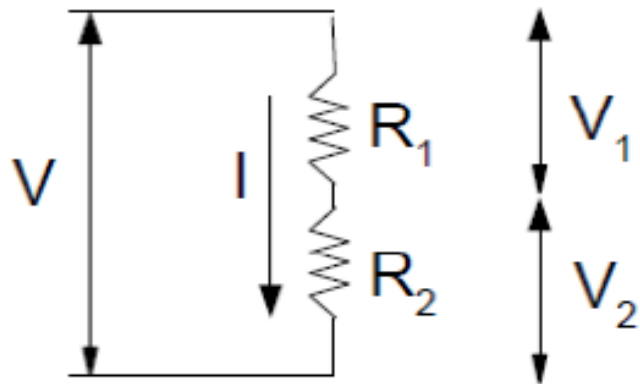


in series

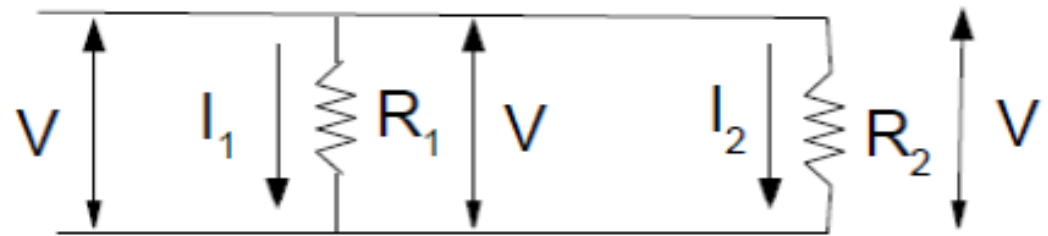


in parallel

# Parallel and series connections

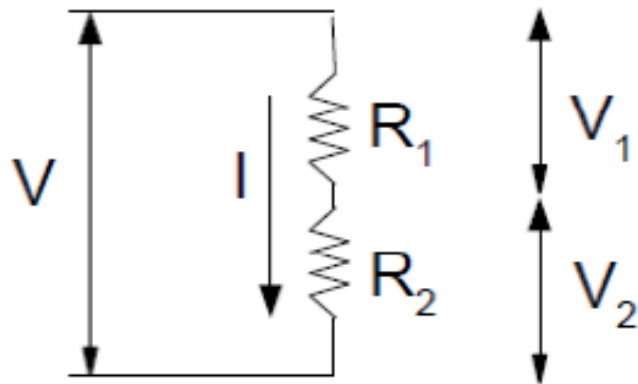


in series

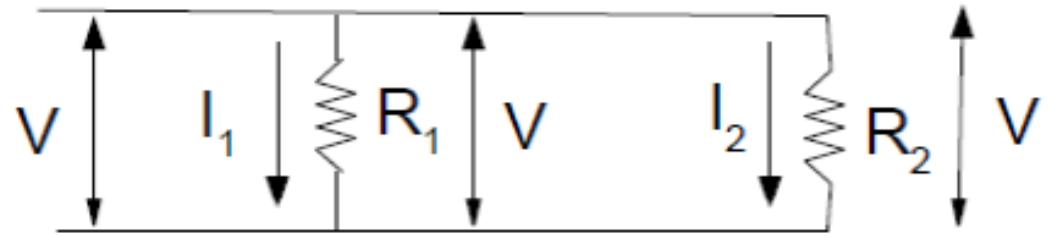

in parallel


**Currents** are the same for the two resistor

# Parallel and series connections

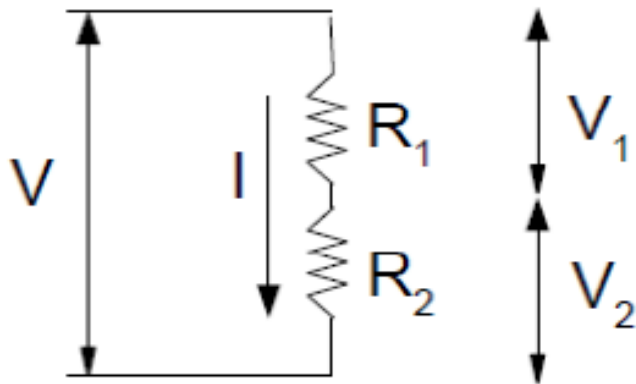

in series

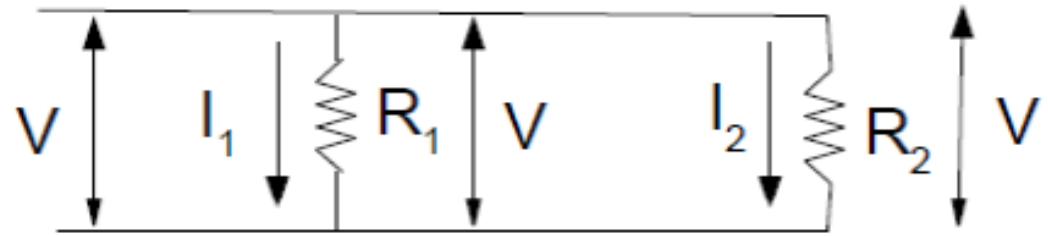
**Currents** are the same for the two resistor




in parallel

**Potential drop** are the same for the two resistor

# Parallel and series connections

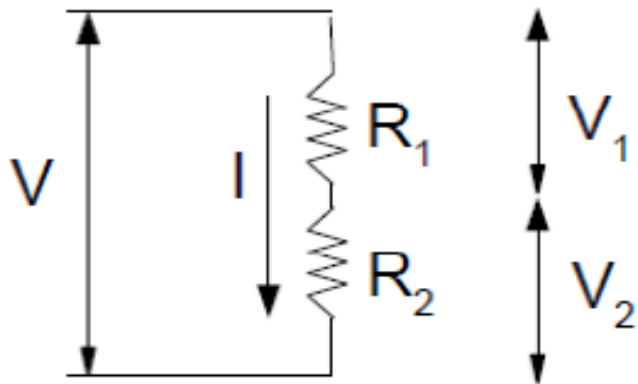


in series

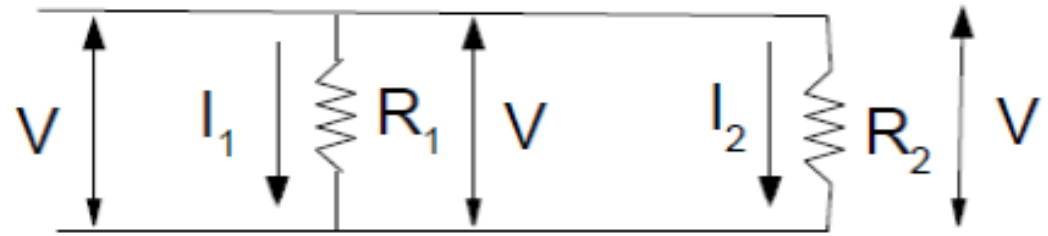


in parallel

$$R_{eq} = R_1 + R_2$$

# Parallel and series connections

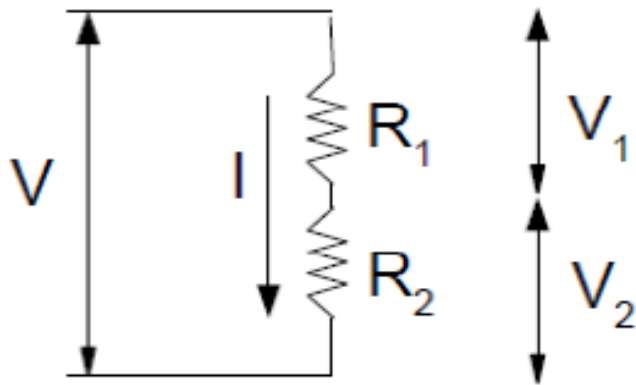

in series

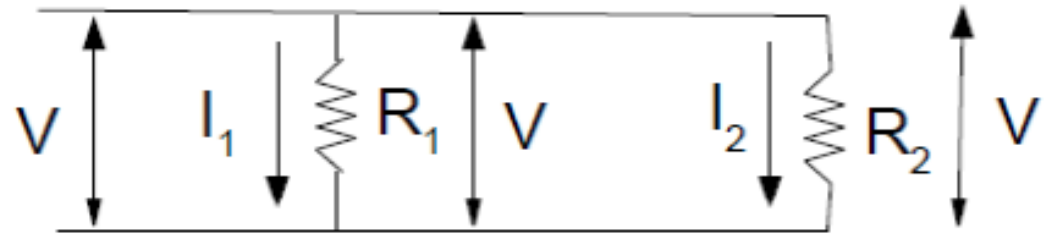


in parallel

$$R_{eq} = R_1 + R_2$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_1}$$

# Example

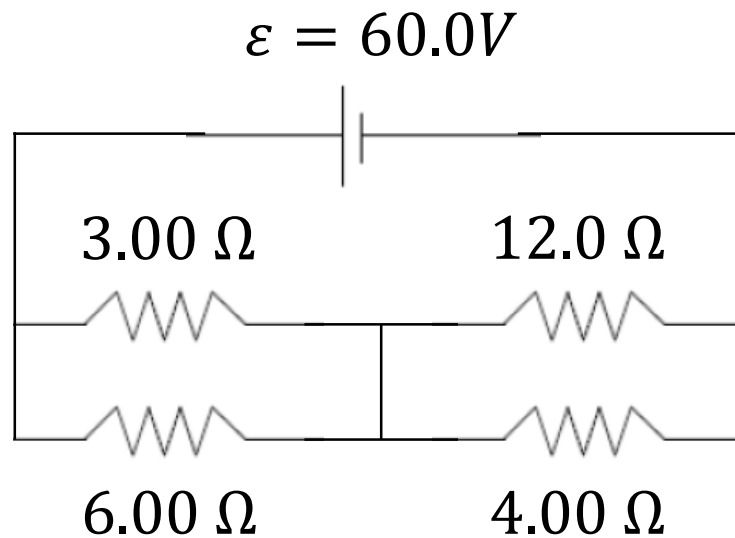


Find  $R_{eq}$ , and the current through each resistor

# Equivalent resistance for complicated circuits

There are complicated circuits which could not be analyzed by the method mentioned above.
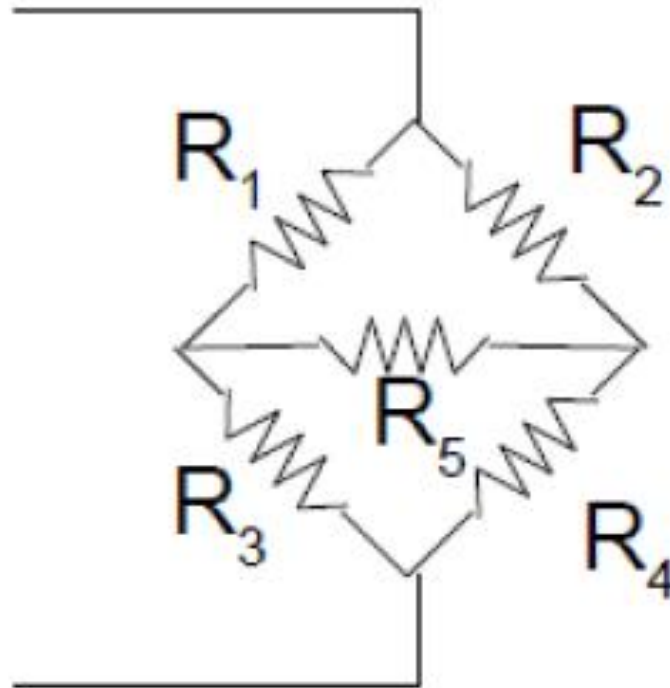
# Equivalent resistance for complicated circuits

There are complicated circuits which could not be analyzed by the method mentioned above.





# The nature of the electric potential and current in circuit

- Current: flow of charge, cannot accumulated at any point in the circuit.

# The nature of the electric potential and current in circuit

- Current: flow of charge, cannot accumulated at any point in the circuit.
- ➔ In same line (path), currents are the same.

# The nature of the electric potential and current in circuit

- Current: flow of charge, cannot accumulated at any point in the circuit.
  - ➔ In same line (path), currents are the same.
  - ➔ At a junction, “flow in” = “flow out”

# The nature of the electric potential and current in circuit

- Current: flow of charge, cannot accumulated at any point in the circuit.
  - ➔ In same line (path), currents are the same.
  - ➔ At a junction, “flow in” = “flow out”
- Potential: related to energy. Drops when pass through a resistance along the direction of the current; increase when pass through a emf source along the direction of current

# The nature of the electric potential and current in circuit

- Current: flow of charge, cannot accumulated at any point in the circuit.
  - ➔ In same line (path), currents are the same.
  - ➔ At a junction, “flow in” = “flow out”
- Potential: related to energy. Drops when pass through a resistance along the direction of the current; increase when pass through a emf source along the direction of current
  - ➔ In ideal wire, no resistance passed, no potential drop (same potential)

# The nature of the electric potential and current in circuit

- Current: flow of charge, cannot accumulated at any point in the circuit.
  - ➔ In same line (path), currents are the same.
  - ➔ At a junction, “flow in” = “flow out”
- Potential: related to energy. Drops when pass through a resistance along the direction of the current; increase when pass through a emf source along the direction of current
  - ➔ In ideal wire, no resistance passed, no potential drop (same potential)
  - ➔ When go through a loop (any loop), the potential change is 0.

# Kirchhoff's rules (for complicated circuit analysis)

**Junction rule** (about current):  $\Sigma I = 0$  at any junction

# Kirchhoff's rules (for complicated circuit analysis)

**Junction rule** (about current):  $\Sigma I = 0$  at any junction

- Flow **into** the junction: **positive**
- Flow **out of** the junction: **negative**



# Kirchhoff's rules (for complicated circuit analysis)

**Junction rule** (about current):  $\Sigma I = 0$  at any junction

- Flow **into** the junction: **positive**
- Flow **out of** the junction: **negative**

**Loop rule** (about current):  $\Sigma V = 0$  for any closed loop

# Kirchhoff's rules (for complicated circuit analysis)

**Junction rule** (about current):  $\Sigma I = 0$  at any junction

- Flow **into** the junction: **positive**
- Flow **out of** the junction: **negative**

**Loop rule** (about current):  $\Sigma V = 0$  for any closed loop

- Potential **drop**: **negative**
- Potential **increase (pump)**: **positive**

# Kirchhoff's rules (for complicated circuit analysis)

Strategy:

1. Define **currents values** and **directions** at each section of path in the circuit.

# Kirchhoff's rules (for complicated circuit analysis)

Strategy:

1. Define **currents values** and **directions** at each section of path in the circuit.
2. Use **junction rule** for each junction in the circuit. Each junction will give one equation.

# Kirchhoff's rules (for complicated circuit analysis)

## Strategy:

1. Define **currents values** and **directions** at each section of path in the circuit.
2. Use **junction rule** for each junction in the circuit. Each junction will give one equation.
3. Choose any certain point as **starting point**, then choose a travel route to complete a **close loop** (your choice, and has to go back to the starting point)

# Kirchhoff's rules (for complicated circuit analysis)

## Strategy:

1. Define **currents values** and **directions** at each section of path in the circuit.
2. Use **junction rule** for each junction in the circuit. Each junction will give one equation.
3. Choose any certain point as **starting point**, then choose a travel route to complete a **close loop** (your choice, and has to go back to the starting point)
4. Use **loop rule** to construct electric potential equation for the loop you chose. (if the travel direction is the same with the current direction, the potential will drop; if opposite, the potential will raise).

# Kirchhoff's rules (for complicated circuit analysis)

## Strategy:

1. Define **currents values** and **directions** at each section of path in the circuit.
2. Use **junction rule** for each junction in the circuit. Each junction will give one equation.
3. Choose any certain point as **starting point**, then choose a travel route to complete a **close loop** (your choice, and has to go back to the starting point)
4. Use **loop rule** to construct electric potential equation for the loop you chose. (if the travel direction is the same with the current direction, the potential will drop; if opposite, the potential will raise).
5. Choose different closed loop which covers **sections that were not covered by other loops** (Some part of the route could be the same). Repeat step 4 until you cover all sections in the circuit)


# Kirchhoff's rules (for complicated circuit analysis)

## Strategy:

1. Define **currents values** and **directions** at each section of path in the circuit.
2. Use **junction rule** for each junction in the circuit. Each junction will give one equation.
3. Choose any certain point as **starting point**, then choose a travel route to complete a **close loop** (your choice, and has to go back to the starting point)
4. Use **loop rule** to construct electric potential equation for the loop you chose. (if the travel direction is the same with the current direction, the potential will drop; if opposite, the potential will raise).
5. Choose different closed loop which covers **sections that were not covered by other loops** (Some part of the route could be the same). Repeat step 4 until you cover all sections in the circuit)
6. Solve the unknown values using the equations constructed by junction rules and loop rules.



# Example

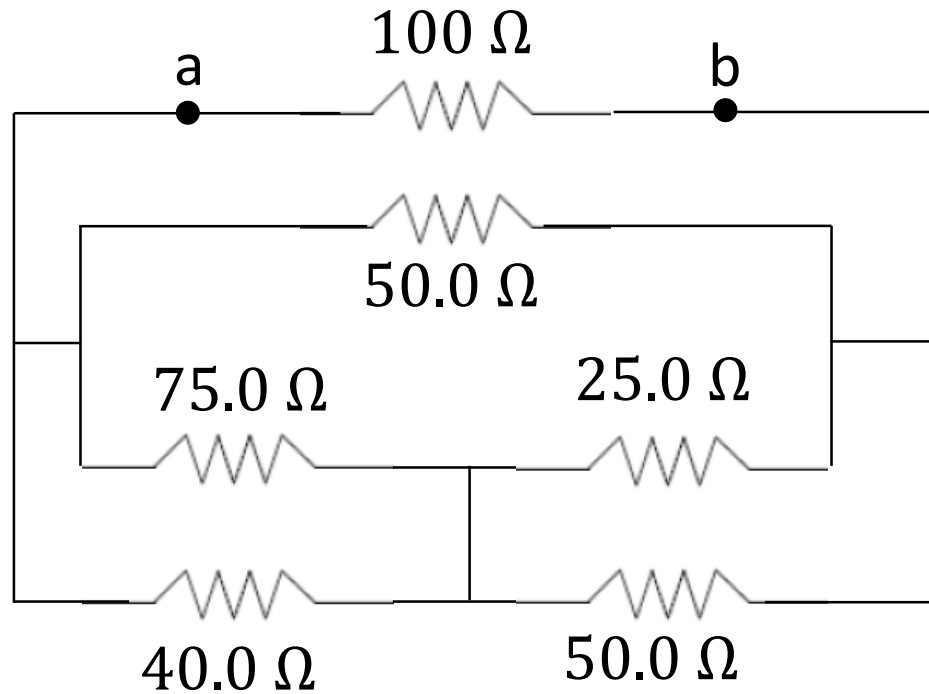

If an ohmmeter is connected between points a and b, what will it read?