

Problem 23.68

A disk with radius R has uniform surface charge density σ .

Part A

By regarding the disk as a series of thin concentric rings, calculate the electric potential V at a point on the disk's axis a distance x from the center of the disk. Assume that the potential is zero at infinity. (*Hint:* Use the result that potential at a point on the ring axis at a distance x from the center of the ring is $V = \frac{1}{4\pi\epsilon_0} \frac{Q}{\sqrt{x^2+a^2}}$ where Q is the charge of the ring and a is the radius of the ring.)

Part B


Calculate $-\partial V/\partial x$.

Problem 23.20.

A positive charge $+q$ is located at the point $x = 0, y = -a$, and a negative charge $-q$ is located at the point $x = 0, y = +a$. (a) Derive an expression for the potential V at points on the y -axis as a function of the coordinate y . Take V to be zero at an infinite distance from the charges. (b) Graph V at points on the y -axis as a function of y over the range from $y = -4a$ to $y = +4a$. (c) Show that for $y > a$, the potential at a point on the positive y -axis is given by $V = -\left(\frac{1}{4\pi\epsilon_0}\right) \frac{2qa}{y^2}$.

Problem 24.12

Three capacitors, with capacitances $C_1 = 2.2 \mu\text{F}$, $C_2 = 2.9 \mu\text{F}$, and $C_3 = 4.6 \mu\text{F}$, are connected to a 18 V voltage source, as shown in the figure. What is the charge on capacitor C_2 ?

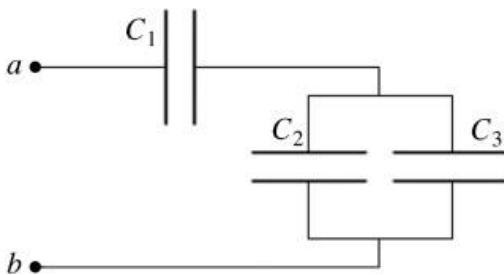

Problem 24.17

The network shown in the figure is assembled with uncharged capacitors X , Y , and Z , with $C_X = 3 \mu\text{F}$, $C_Y = 6 \mu\text{F}$, and $C_Z = 7 \mu\text{F}$ and open switches, S_1 and S_2 . A potential difference $V_{ab} = +120 \text{ V}$ is applied between points a and b . After the network is assembled, switch S_1 is closed for a long time, but switch S_2 is kept open. Then switch S_1 is opened and switch S_2 is closed. What is the final voltage across capacitor X ?

