


ch09/s6.html

Q#1 \square equally bright since they have the same current and R

$$P_A = I^2 R = P_B$$

Q#2 \square The current in Circuit b is 2x greater, so $P = I^2 R$ means 4x brighter

Example

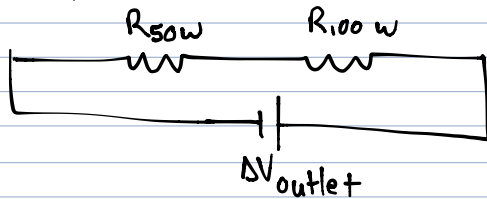

What is the current?

Assume 120 V

You may combine into one equivalent resistor, but you still need their

individual resistances to do that

$$P_{50w} = \frac{V^2}{R_{50w}} = \frac{(120V)^2}{R_{50w}}$$

$$\Rightarrow R_{50w} = \frac{(120V)^2}{50W} = 288 \Omega$$

step

$$R_{100w} = \frac{(120V)^2}{100W} = 144 \Omega$$

$$\rightarrow R_{eq} = 288 \Omega + 144 \Omega = 432 \Omega$$

$$I = \frac{V}{R_{eq}} = \frac{120V}{432 \Omega} = 280mA$$

In parallel, resistances add inversely $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

ch10 s1.html


Adding more resistors drops R_{eq}

s2.html (A)

s3.html Bulb B is short-circuited \Rightarrow B goes out and A now has 2x the current

$$\Rightarrow P_A = (2I)^2 R_A = 4I^2 R_A = 4 P_A$$

full example

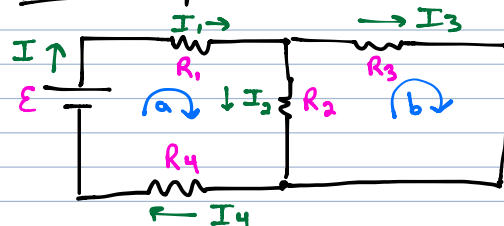

What is I through the battery?

- Draw diagram; label!
- Use junction rule to eliminate extraneous current subscripts
- loop through all mini-loops until all elements covered

$$\text{eq}^n \text{ a) } \sum \Delta V = 0 : \mathcal{E} - I_1 R_1 - I_2 R_2 - I R_4 = 0$$

$$\text{eq}^n \text{ b) } \sum \Delta V = 0 : -I_3 R_3 + I_2 R_2 = 0$$

$$\text{eq}^n \text{ c) } \sum I = 0 \text{ at any junction : } I = I_2 + I_3$$