

Finish the last circuit

$$a) I_2 = \frac{E - I(R_1 + R_4)}{R_2}$$

$$b) I_3 = I_2 \frac{R_2}{R_3} = \frac{E - I(R_1 + R_4)}{R_2} \frac{R_2}{R_3} = \frac{E - I(R_1 + R_4)}{R_3}$$

$$c) I = \frac{E - I(R_1 + R_4)}{R_2} + \frac{E - I(R_1 + R_4)}{R_3} \Rightarrow I = \frac{E(R_2 + R_3)}{R_2 R_3 + (R_1 + R_4)(R_2 + R_3)}$$

$$E = 12V \quad R_1 = R_2 = 20\Omega \quad R_3 = 30\Omega \quad R_4 = 80\Omega$$

$$I = 0.107A$$

It's much easier to first combine  $R_2$  &  $R_3$ :  $R_{23} = \frac{R_2 R_3}{R_2 + R_3}$

$$R_{eq} = R_1 + R_{23} + R_4 \Rightarrow I = \frac{V}{R_{eq}}$$

Suppose  $R_4 \gg R_1, R_2, R_3$

$$I = \frac{E \frac{R_2 + R_3}{R_4 \frac{R_2 R_3}{R_2 + R_3} + (R_1 + R_4)(R_2 + R_3)}}{\frac{R_2 + R_3}{R_4}} \approx \frac{E}{R_4}$$

Suppose  $R_1 = R_2 = R_3 = R_4 \equiv R$  and you want to maximize battery life.

If you could remove one  $R$ , which would it be?

$$P = E^2 / R_{eq} \quad \text{minimizing } P \Rightarrow \text{maximizing } R_{eq}$$

$$R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3} + R_4$$

$$\text{removing } R_1 \text{ or } R_4 \Rightarrow R_{eq} = \frac{3}{2}R$$

$$\text{removing } R_2 \text{ or } R_3 \Rightarrow R_{eq} = 3R$$

Practice Problem

Find  $\vec{E}$  and the charge distributions



