

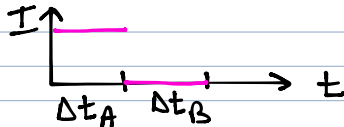
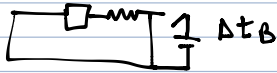


ch10 s9.html RC circuit intro

option c


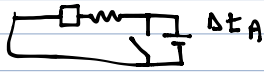


option b

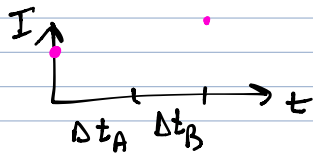

no resistance \rightarrow C can charge and discharge immediately

option a

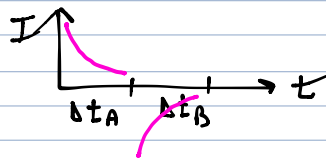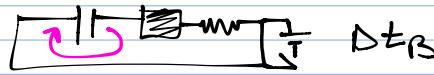

In Δt_A , charge builds up on capacitor ($I \neq 0$)
 $V_c(t) = q(t)/C$ until at some much later time t_f

$$V_c(t_f) \approx \frac{Q_f}{C} \quad (I=0)$$

"loop it": $\sum \Delta V = 0 = \mathcal{E} - i(t)R - \frac{q(t)}{C}$

using $i(t) = \frac{dq(t)}{dt}$: $\mathcal{E} - \frac{dq(t)}{dt}R - \frac{q(t)}{C} = 0$






$\rightarrow q(t) = C\mathcal{E}(1 - e^{-t/RC})$ charging capacitor in RC circuit

does it work? $q(0) = C\mathcal{E}(1-1) = 0 \checkmark$




$q(t_f \rightarrow \infty) = C\mathcal{E}(1-0) = C\mathcal{E} \checkmark$


what is current? $i(t) = \frac{dq}{dt} = C\mathcal{E} \left(0 + \frac{1}{RC} e^{-t/RC} \right)$

It's 4:00 pm on October 31, and you just realized that it was your job to contribute the scary sound for this year's haunted house.
Supplies at hand:

-  resistor
-  capacitor
-  12 V battery
-  copper wire
-  speaker - 50 Hz and 70 db (scary!)

For optimal scariness, you should modulate the sound by repeatedly opening and closing:

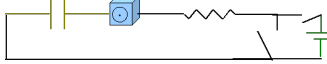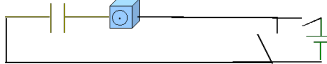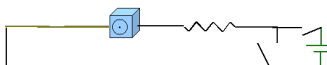- a) 
- b) 
- c) 

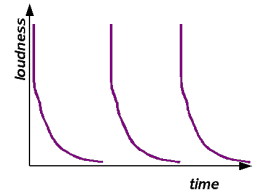

does this work? $i(0) = \frac{\epsilon}{R} e^{-0} = \frac{\epsilon}{R} = I_0 \checkmark$

$$i(t \rightarrow \infty) = \frac{\epsilon}{R} e^{-\infty} = 0 \checkmark$$

During Δt_B

"loop it": $-iR - \frac{q}{C} = 0 \Rightarrow i(t) = -\frac{q(t)}{RC} \Rightarrow \frac{dq}{dt} = -\frac{q}{RC}$

$$Q \int \frac{dq'}{q'} = \int_0^t -\frac{dt'}{RC} \Rightarrow \ln \frac{q}{Q} = -\frac{t}{RC} \Rightarrow q = Q e^{-t/RC}$$

$$\Rightarrow i = dq/dt = -\frac{Q}{RC} e^{-t/RC}$$

ch 10 s4.html C

ch 10 s6.html B

ch 10 s7.html C

Example

a)

loop it $\epsilon - I_1 R_1 + \epsilon_2 - I_2 R_2 = 0$

$$I_1 = I_2 \Rightarrow I_1 = \frac{\epsilon_1 + \epsilon_2}{R_1 + R_2} = 0.229 \text{ A}$$


if $V_b = 0$, $V_a = 25\text{V} - 0.229 \text{ A} (100\Omega)$

$$= 2.15 \text{ V}$$

a is higher

26.33 • In the circuit shown in Fig. E26.33 all meters are idealized and the batteries have no appreciable internal resistance. (a) Find the reading of the voltmeter with the switch S open. Which point is at a higher potential: a or b ? (b) With S closed, find the reading of the voltmeter and the ammeter. Which way (up or down) does the current flow through the switch?

Figure E26.33

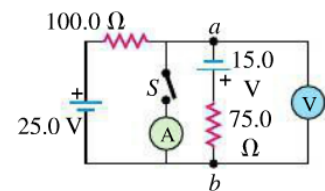

b) two mini-loops

i) $\epsilon_1 - I_1 R_1 = 0 \rightarrow I_1 = \epsilon_1 / R_1 = 0.25 \text{ A}$

ii) $\epsilon_2 - I_2 R_2 = 0 \rightarrow I_2 = \epsilon_2 / R_2 = 0.20 \text{ A}$

$$I_{\text{thru ammeter}} = I_2 - I_1 = 0.20 - 0.25 \text{ A} = -0.05 \text{ A} \text{ (flowing downward)}$$