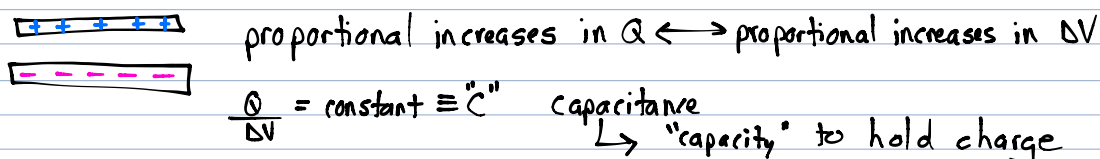


Chapter 08 - Capacitance


From the "Charges and Fields" PhET simulation we saw that $\Delta V \propto Q$ on plate



$$\frac{Q}{\Delta V} = \text{constant} \equiv "C" \quad \text{capacitance}$$

\rightarrow "capacity" to hold charge

Some basics:

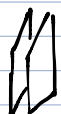


Take a pair of parallel conducting slabs. Hook up a battery



\leftarrow conducting wires

battery ΔV

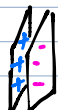

Remove the battery \rightarrow charges are held apart \Rightarrow potential energy is stored

Q: How can we retrieve this U ?

A: Put a charge between the plates - it will move

A: hook up a light bulb \rightarrow negative charges move toward the positive charges
via the conducting wire \rightarrow bulb glows

Q: How can we increase the stored charge?


A: Increase plate area



\leftarrow conducting wires


battery ΔV

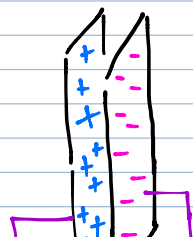only so many charges can hop onto the plates
before "Coulombic saturation"





more area, more charge

$$\rightarrow C \propto A$$

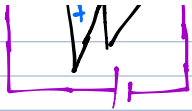

same battery, same ΔV


A: move plates closer together

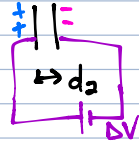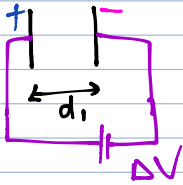

I haven't changed the battery, yet there is more attraction between charges

$$C \propto \frac{1}{d}$$

A: Place an insulator between plates

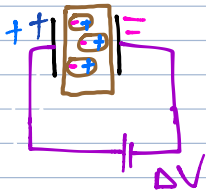


the atoms within the insulator do not move by definition, but they can rotate

$$C \propto K$$

2 identical capacitors in series

concept question ch08/sl.html

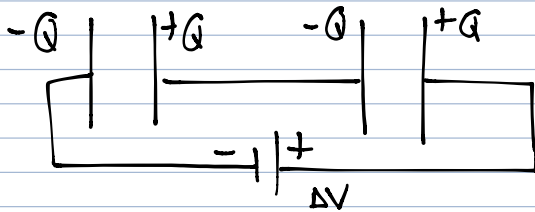

answer = a

Concept Question follow-up

How does the magnitude of the charge change?

Can answer in two ways

i) conceptually, inserting dielectric increases capacitance $\Rightarrow Q = C \Delta V$ means more charge

ii) quantitative

Case a
potential difference on each plate is $\Delta V/2$

$$Q = C_1 \Delta V_1 = C_2 \Delta V_2 = C_1 \frac{\Delta V}{2} = C_2 \frac{\Delta V}{2}$$


$$\text{also, } \Delta V = \Delta V_1 + \Delta V_2 = \frac{Q}{C_1} + \frac{Q}{C_2} \rightarrow \frac{\Delta V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} \equiv \frac{1}{C_{eq}} \Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

if $C_1 = C_2$, then $C_{eq} = \frac{1}{2} C$

$\rightarrow Q = C_{eq} \Delta V = \frac{C}{2} \Delta V$ for $C_1 = C_2 = C$

case b: $C_{eq} = \frac{KC^2}{KC+C} = \frac{KC}{K+1} = \frac{C}{\frac{1}{K}+1} > \frac{C}{2}$ i.e. $C_{case b} > C_{case a}$

Capacitors in parallel

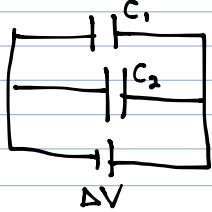

Now the capacitors have the same voltage drop


We know $\Delta V = \Delta V_1 = \Delta V_2$
 $\frac{Q}{C_{eq}} \quad \frac{Q}{C_1} \quad \frac{Q}{C_2}$

Also, $Q_{total} = Q_1 + Q_2 = C_1 \Delta V_1 + C_2 \Delta V_2 = C_1 \Delta V + C_2 \Delta V = (C_1 + C_2) \Delta V$


$\rightarrow C_1 + C_2 = Q / \Delta V \Rightarrow C_{eq} = C_1 + C_2$

Group work


Find C_{eq} for:

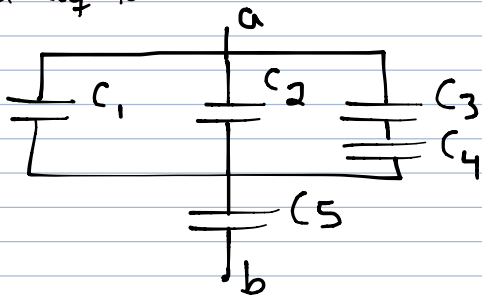

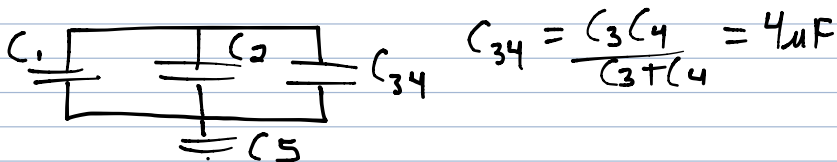$C_1 = 3 \mu F$ $C_2 = 11 \mu F$ $C_3 = 12 \mu F$ $C_4 = 6 \mu F$
 $C_5 = 9 \mu F$



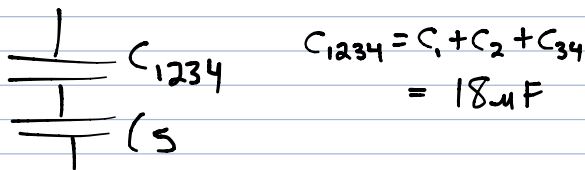$C_{34} = \frac{C_3 C_4}{C_3 + C_4} = 4 \mu F$



$C_{1234} = C_1 + C_2 + C_{34}$
 $= 18 \mu F$

$\frac{1}{C_{12345}} = \frac{1}{C_{1234}} + \frac{1}{C_5} = 6 \mu F$