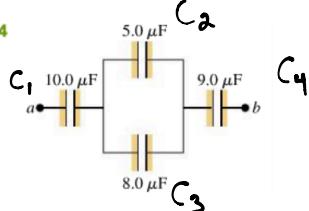


## Practice problems on combining capacitors


### 24.14 from ch08 Tutorials

**24.14** • Figure E24.14 shows a system of four capacitors, where the potential difference across  $ab$  is 50.0 V. (a) Find the equivalent capacitance of this system between  $a$  and  $b$ . (b) How much charge is stored by this combination of capacitors? (c) How much charge is stored in each of the 10.0- $\mu\text{F}$  and the 9.0- $\mu\text{F}$  capacitors?


Figure E24.14



a)  $3.47 \mu\text{F}$

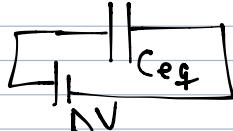

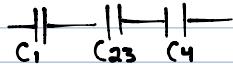
$$C_2 \text{ & } C_3 \text{ in parallel} \rightarrow C_{23} = C_2 + C_3 = 13 \mu\text{F}$$




$$\text{in series} \rightarrow C_{1234} \neq \frac{C_1 C_{23} C_4}{C_1 + C_{23} + C_4}$$
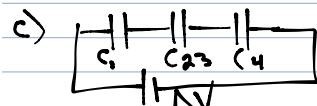
$$C_{1234} = \left[ \frac{1}{C_1} + \frac{1}{C_{23}} + \frac{1}{C_4} \right]^{-1} = 3.47 \mu\text{F}$$


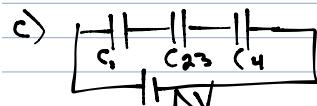
$$Q = C_{eq} \Delta V = 173.5 \mu\text{C}$$




in series,  $Q_{tot}$  for  $C_{eq}$  is the same as the individual  $Q$ 's

$$\Rightarrow 173.5 \mu\text{C}$$

**24.16** • For the system of capacitors shown in Fig. E24.16, find the equivalent capacitance (a) between  $b$  and  $c$ , and (b) between  $a$  and  $c$ .

Figure E24.16

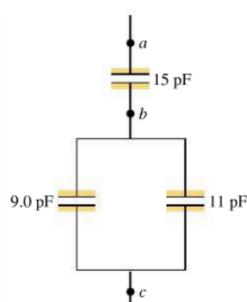


$$\frac{\frac{1}{C_1} + \frac{1}{C_{23}}}{\frac{1}{C_1} + \frac{1}{C_{23}} + \frac{1}{C_4}} \text{ where } C_{23} = 9.0 \text{ pF} + 11 \text{ pF} = 20 \text{ pF}$$

$$C_{123} = \left( \frac{1}{C_1} + \frac{1}{C_{23}} \right)^{-1} = 8.6 \text{ pF}$$

**24.17** • In Fig. E24.17, each capacitor has  $C = 4.00 \mu\text{F}$  and  $V_{ab} = +28.0 \text{ V}$ . Calculate (a) the charge on each capacitor; (b) the potential difference across each capacitor; (c) the potential difference between points  $a$  and  $d$ .

**24.18** • In Fig. 24.8a, let  $C_1 = 3.00 \mu\text{F}$ ,  $C_2 = 5.00 \mu\text{F}$ , and  $V_{ab} = +64.0 \text{ V}$ . Calculate

Figure E24.17

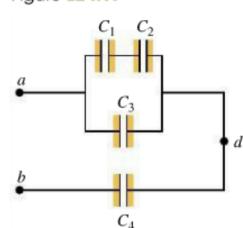

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2} = 2 \mu\text{F}$$


$$C_{123} = C_1 + C_2 + C_3 = 6 \mu\text{F}$$

$$C_{1234} = \left( \frac{1}{C_{123}} + \frac{1}{C_4} \right)^{-1} = 2.4 \mu\text{F}$$

$$Q = C_{eq} V = 2.4 \mu F \cdot 28.0 V = 67.2 \mu C$$

$$Q_4 = 67.2 \mu C = Q_{123}$$

backing up:

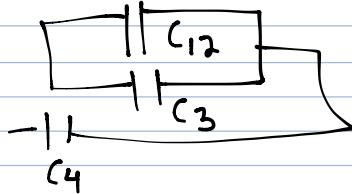

$$67.2 \mu C = Q_{12} + Q_3 = C_{12} V_{12} + C_3 V_3$$

$$\text{where } V_{12} = V_3$$

$$V_{tot} = 28 V = V_4 + V_{123} \quad (V_{123} = V_{12} = V_3)$$

$$V_4 = Q_4 / C_4 = 67.2 \mu C / 4 \mu F = 16.8 V \Rightarrow V_{123} = V_3 = V_{12} = 28 V - 16.8 V = 11.2 V$$

$$C_3 = Q_3 / V_3 =$$

$$Q_3 = C_3 V_3 = 4 \mu F (11.2 V) = 44.8 \mu C$$

Concept Q ch08/53.html

(b) parallel  $\rightarrow$  same  $\Delta V$ !

follow-up: What are their new  $\Delta V$ 's and  $Q$ 's?  $Q'_3$  and  $Q'_4$

$$\begin{array}{c} \text{C}_3 \\ \parallel \\ \text{C}_4 \end{array} \quad V_B - V_C \quad C_{eq} = C'_3 + C'_4 = C_3 + C_4 \quad \text{since } C_3 = C'_3 \quad C_4 = C'_4$$

$$Q_{total} = Q'_3 + Q'_4 = Q_3 + Q_4 \quad \text{cons. of charge}$$

$$\text{and since } \frac{Q_{total}}{C_{eq}} = \Delta V \quad \because \Delta V = V_B - V_C = V_A - V_D \rightarrow V_B - V_C = \frac{Q_3 + Q_4}{C_3 + C_4}$$

$$Q'_3 = C'_3 (V_B - V_C) = C_3 \frac{Q_3 + Q_4}{C_3 + C_4}$$


$$Q'_4 = C'_4 (V_A - V_D) = C_4 \frac{Q_3 + Q_4}{C_3 + C_4}$$

Numbers: Suppose  $C_3 = 2 \mu F$      $C_4 = 4 \mu F$   
 $Q_3 = 24 \mu C$      $Q_4 = 12 \mu C$   
 $\Delta V_3 = 12 V$      $\Delta V_4 = 3 V$

$$\begin{aligned} \rightarrow Q'_3 &= 2 \mu F \frac{36 \mu C}{6 \mu F} \\ &= 12 \mu C \end{aligned} \quad \begin{aligned} Q'_4 &= 4 \mu F \frac{36 \mu C}{6 \mu F} \\ &= 24 \mu C \end{aligned}$$

$$Q'_3 + Q'_4 = 36 \mu C = Q_3 + Q_4 \quad \checkmark$$

### Energy storage in capacitors

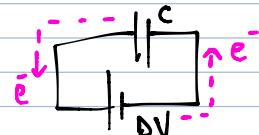

At some time  $t$ , charge on plates is  $q$

To transfer charge  $dq$  from one plate to another,

$$\text{requires } dW = DV dq = \frac{q}{C} dq$$

$$\text{Total work to transfer } Q \text{ is } W = \int dW = \int \frac{q}{C} dq = \frac{1}{C} \int dq q$$


$$= \frac{1}{2} \frac{Q^2}{C}$$

How long can we illuminate a light bulb that generates 2.4 Watts when connected to a  $450,000\text{-}\mu\text{F}$  capacitor and  $4.5\text{V}$ ?

energy stored in capacitor is  $\frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} 450,000\text{-}\mu\text{F} \cdot (4.5\text{V})^2 = 4.6\text{ J}$

$$\Delta t = \frac{\text{energy stored}}{\text{energy loss rate}} = \frac{4.6\text{ J}}{2.4\text{ W}} = 1.9\text{ s}$$

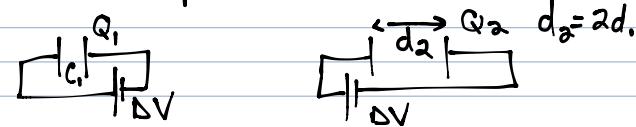Take two capacitors, one with separation  $d$  of the plates, and one with separation  $2d$



$$C \propto \frac{1}{d}$$

$$C_1 = 2C_2$$

If  $\Delta V_1 = \Delta V_2$ , then

$$Q_1 = 2Q_2 \rightarrow U_1 = \frac{1}{2} \frac{Q_1^2}{C_1} = \frac{1}{2} \frac{4Q_2^2}{2C_2} = 2 \left( \frac{1}{2} \frac{Q_2^2}{C_2} \right) = 2U_2$$


Portable heart defibrillator

$$C = 70\text{-}\mu\text{F} \quad \Delta V = 5000\text{V} \quad U = \frac{1}{2} CV^2 = 875\text{ J}$$

about 200J of this is sent in a  $\sim 2.0\text{ms}$  pulse

$\rightarrow$  Power =  $\frac{\text{energy}}{\text{time}} = 100\text{kW}$  (much greater than the battery could provide)

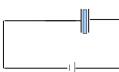Suppose a dielectric placed between two plates of a capacitor increases the overall capacitance by a factor of two.



$$U = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} QV$$

The amount of stored energy in the capacitor

- a) doubles
- b) halves
- c) quadruples
- d) is four times smaller