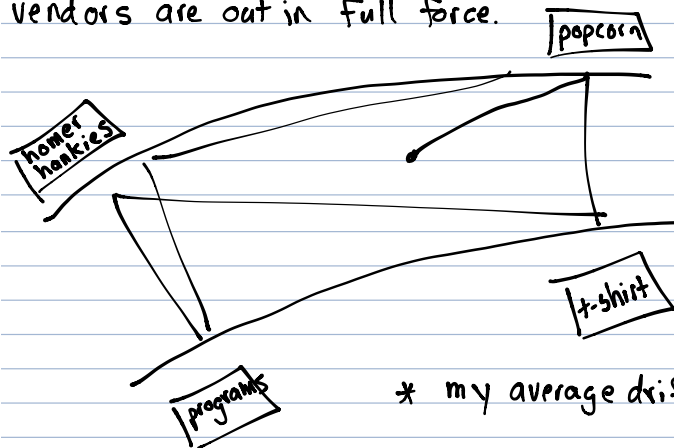


# Current & Resistivity

Setting: The Metrodome (Minneapolis)  
 Oct 1987  
 3 hours before Game 2 of WS



I'm the only fan wandering the stadium corridors. But of course the vendors are out in full force.



I frantically try to snap up every souvenir possible, and food items, before the hordes arrive.

My typical unimpeded speed is  $10^6$  m/s  
 \* 2 hours later, the crowd arrives.

\* my average drift velocity is  $v_d \sim 0$  m/s


The 1st pitch nears; I frantically make my way to my seat.

I'm finding it difficult to make my way

my  $v_d$  is now  $\sim 10^{-4}$  m/s, but I'm still moving at  $10^6$  m/s

The "field" pushes me to my seat.

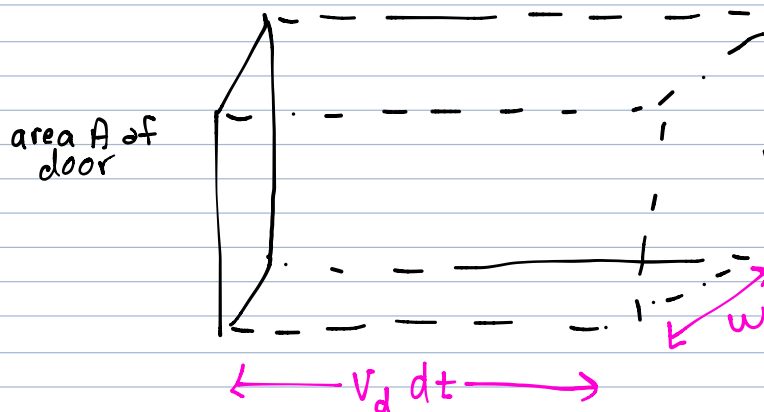The "people current" - how many people pass thru a door of width  $w$  in time  $dt$



people in this volume

$$\text{is } \frac{\text{people} \cdot \text{volume}}{\text{volume}}$$

$$= \frac{\text{people}}{\text{volume}} \cdot v_d dt A$$

$\rightarrow$  people/time = people current

$$= \frac{\text{people}}{\text{volume}} \cdot v_d \cdot A$$


at the atomic level, faster speeds  $\leftrightarrow$  increased  $T$

$$\rho(T) \propto \text{change in } T: \rho(T) = \rho_0 + \rho_0 \alpha (T - T_0)$$


$\rho \uparrow$



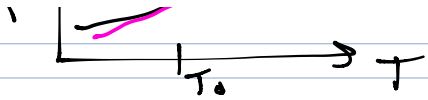The relation isn't perfectly linear, but it's a



good approximation for most T

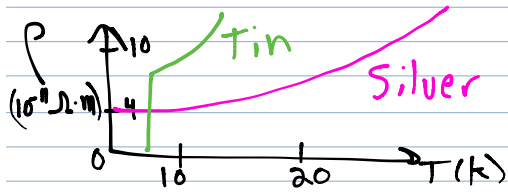

$T_{critical}$  for  $S_b$  is  $\sim 4K$

Q: Why does a light bulb turn on "instantly", though  $v_d \sim 10^{-4} m/s$ ?

A: Only need  $e^-$  at one end to move just into the wiring (think of water filling a hose)

Resistivity and Resistance

Resistance  $R \propto \rho$


Resistance  $R \propto L$  length

Resistance  $R \propto \frac{1}{A}$   $\rightarrow R = \frac{\rho L}{A}$

Also, think of "how much flow" vs "how much push"

Ohm's Law  $R = \frac{V}{I}$

DC circuits

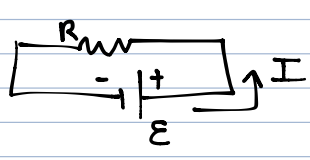


$R$  = resistance of resistor  
 $\epsilon$  = potential provided by battery  
 $I$  = current

$I = \epsilon / R$

Q: How does a battery provide a potential difference?

A: chemical reactions occur that separate charges

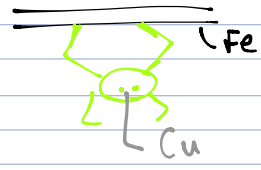
Luigi Galvani in 1786 suspended a frog from an iron rod




induced muscle twitching

$\rightarrow$  discovered frogs are moist conductors

A more realistic circuit:

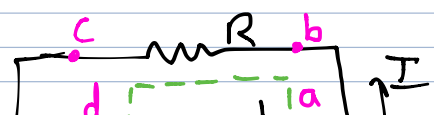

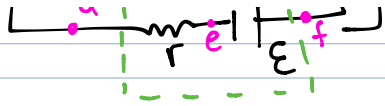Important rule: if a charge starts at one location, traverses the circuit and returns



to its starting point, then  $\oint \Delta V = 0$   
 $\rightarrow$  total change in electrical P.E. is zero

$$V_a = \epsilon$$

$$V_e = V_d - Ir = \epsilon - IR - Ir$$

$$V_b = V_a = \epsilon$$

$$V_f = V_e + \epsilon = 2\epsilon - IR - Ir$$

$$V_c = V_b - IR = \epsilon - IR$$

$$\text{Also, } V_f = V_a = \epsilon \Rightarrow 2\epsilon - IR - Ir = \epsilon \Rightarrow I = \frac{\epsilon}{R+r}$$


$$V_d = V_c = \epsilon - IR$$

Concept Q ch09/sl.html (A)

$$R_{\text{diff}} = \frac{V}{I} = \frac{20V}{20mA} = 1000 \Omega$$

$$100mA \cdot 1000\Omega = V = 100V$$

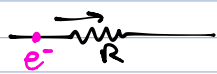Power energy is transferred when a current passes through a resistor. But at what rate?



Work to push charge through  $\Delta V dq$

$$d\text{Power} = \frac{dW}{dt} = \frac{\Delta V dq}{dt} = \Delta V \frac{dq}{dt} = \Delta V I$$

$$P = IV = I(IR) = I^2 R = V^2/R$$

ch09/s2.html (B)

$V = \text{same}$

$$P_{100}/P_{50} = 2 = \frac{V^2/R_{100}}{V^2/R_{50}} = R_{50}/R_{100}$$

ch09/s3.html (A)

They have the same current, so use  $P = I^2 R$

$$P_{50}/P_{100} = \frac{I^2 R_{50}}{I^2 R_{100}} = \frac{R_{50}}{R_{100}} = 2$$

25.29 • When switch  $S$  in Fig. E25.29 is open, the voltmeter  $V$  reads 3.08 V. When the switch is closed, the voltmeter reading drops to 2.97 V, and the ammeter  $A$  reads 1.65 A. Find the emf, the internal resistance of the battery, and the circuit resistance  $R$ . Assume that the two meters are ideal, so they don't affect the circuit.

Figure E25.29

