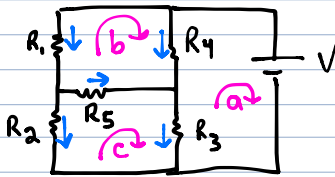


$$R_{eq} = ((6+3)^{-1} + (3+6)^{-1})^{-1} = 4.5 \Omega$$

$$\rightarrow I_{\text{thru battery}} = \frac{36V}{4.5\Omega} = 8A$$

$$V_{ab} = V_a - V_b = 12V - 24V = -12V$$

now close switch



$$a) I_3 R_3 + I_4 R_4 - V = 0$$

We have 5 unknowns (the currents)

$$b) I_1 R_1 - I_4 R_4 + I_5 R_5 = 0$$

→ need 5 eqns

$$c) I_2 R_2 - I_5 R_5 - I_3 R_3 = 0$$

$$i) I_1 = I_2 + I_5$$

$$I_5 = -1.71 A \Rightarrow I \text{ assumed the incorrect direction}$$

$$ii) I_5 + I_4 = I_3$$

$$I_4 = 5.14 A$$


c) what is R_{eq} ?

$$I_1 = 3.42 A$$

$$I_{\text{battery}} = I_4 + I_1 = 8.57 A \Rightarrow R_{eq} = \frac{\mathcal{E}}{I_{\text{battery}}} = 4.2 \Omega$$

28.66 • The wire semicircles shown in **Fig. P28.66** have radii a and b . Calculate the net magnetic field (magnitude and direction) that the current in the wires produces at point P .

Figure **P28.66**

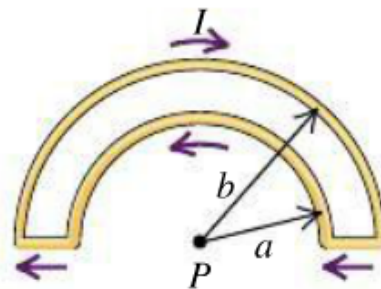

There are two semi-circles that produce B fields (at P) in opposite directions

$$B(\text{at } P)_{\text{due to inner}} = \frac{1}{2} \frac{\mu_0 I}{2a} \hat{k} - \frac{1}{2} \frac{\mu_0 I}{2b} \hat{k}$$

the factors of $\frac{1}{2}$ account for the semi-circles