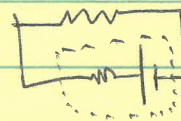


Ch 10 solutions

1

22) a) $I = V/R_{eq} = 12/0.06 = \boxed{200 \text{ A}}$



b) Since $R_{internal} = 0.01 \Omega$, then voltage "wasted" within battery is $IR_{internal} = 20 \text{ V} \Rightarrow \Delta V_{motor} = \boxed{10.0 \text{ V}}$

c) $P = \Delta V^2/R_{motor} = 10^2/0.05 = \boxed{2000 \text{ W}}$

d) $I = 12/0.15 = \boxed{80 \text{ A}}$ $\Delta V_{motor} = 12 \text{ V} - 80 \cdot 0.1 = \boxed{4 \text{ V}}$ $P = 4^2/0.05 = \boxed{320 \text{ W}}$

24)



a) $I = \frac{20,000}{12,000} = \boxed{1.67 \text{ A}}$

b) $P = I^2 R = (1.67)^2 (10,000) = \boxed{2.78 \text{ kW}}$

c) $I_{th} < 10^{-3} \Rightarrow R > V/I_{th} = \boxed{20 \text{ M}\Omega}$

d) From solutions manual: "With low current, the power supply is still effective as power loss is low due to internal resistance."

28) a) $I = P/V \Rightarrow I_{toaster} = \boxed{15 \text{ A}}$ $I_{speaker} = \boxed{11.7 \text{ A}}$ $I_{lamp} = \boxed{0.63 \text{ A}}$

b) $I_{total} = I_{toaster} + I_{speaker} + I_{lamp} > 15 \text{ A}$ yes


33)

a) $\Delta V_1 = 15 \cdot 0.8 = 12 \text{ V}$ $\Delta V_2 = \Delta V_3 = 120 - 12 = 108 \text{ V}$
 $\Rightarrow P_{bulb} = V_3^2/R_2$ where $R_2 = 120^2/75 = 192 \Omega$
 $= 108^2/192 = \boxed{60.75 \text{ W}}$

b) $R_{eq} = 120 \text{ V}/15 \text{ A} = 8 \Omega$
 also, $R_{eq} = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3}\right)^{-1} \Rightarrow R_3 = \left[(R_{eq} - R_1)^{-1} - \frac{1}{R_2}\right]^{-1} = 7.48 \Omega$
 $\Rightarrow P_3 = 108^2/7.48 = \boxed{1559 \text{ W}}$

36) a) $I = \frac{24 \text{ V} - 12 \text{ V}}{60 \cdot 10^3 \Omega} = 0.2 \text{ mA} \Rightarrow \Delta V_1 = 1, R_1 = 2.00 \text{ V}$ $\Delta V_2 = 4.00 \text{ V}$ $\Delta V_3 = 2.00 \text{ V}$
 $\Delta V_4 = 2.00 \text{ V}$ $\Delta V_5 = 2.00 \text{ V}$

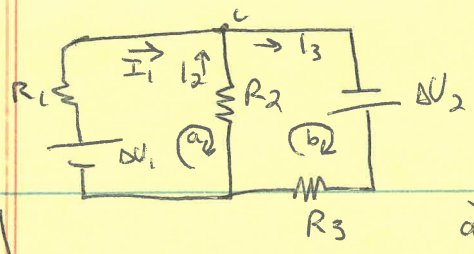b) battery 2 powers the circuit $\Rightarrow P_{in} = I \Delta V_2 = \boxed{1.8 \text{ mW}}$
 $P_{out} = I \Delta V_1 + I^2 (R_1 + R_2 + R_3 + R_4 + R_5) = \boxed{4.8 \text{ mW}}$



38)

a) $\Delta V_1 - I_1 R_1 + I_2 R_2 = 0$
 c) $I_1 + I_2 = I_3$

b) $-I_2 R_2 + \Delta V_2 - I_3 R_3 = 0$

e) $I_2 = I_3 - I_1$ (4)

(4) into (b): $-I_3 R_2 + I_1 R_2 + \Delta V_2 - I_3 R_3 = 0$ (5)

$\Rightarrow I_3 = (I_1 R_2 + \Delta V_2) / (R_2 + R_3) = \frac{12+24}{6+5} = 3 \text{ A}$ (6)

(6) into (4): $I_2 = 3 - 2 = 1 \text{ A}$ (7)

(7) into (a): $\Delta V_1 = I_1 R_1 - I_2 R_2 = 24 - 6 = 18 \text{ V}$

50)

$V_f = V_i (1 - e^{-\Delta t / RC}) \Rightarrow 0.632 = 1 - e^{-\Delta t / RC}$
 $\Rightarrow R = -\Delta t / (C \ln(0.368)) = \frac{-60/72}{25 \cdot 10^{-9} \ln(0.368)} = 3.33 \cdot 10^7 \Omega$

52)

$R_a = 125 \text{ k}\Omega$ $R_b = 20 \text{ k}\Omega$ $C_a = 9.50 \mu\text{F}$ $C_b = 1.5789 \mu\text{F}$
 $\Rightarrow R_a C_a = 1.188 \text{ s}$ $R_a C_b = 0.197 \text{ s}$ $R_b C_a = 0.19 \text{ s}$ $R_b C_b = 0.0316 \text{ s}$

56)

$V(t) = V_f (1 - e^{-t/RC}) \Rightarrow 0.9 = 1 - e^{-t/RC} \Rightarrow t = -RC \ln 0.1 = 17.3 \text{ ms}$

62)

Section 10.6 of OpenStax textbook indicates $< 1 \text{ mA}$ for no sensation
 $\Rightarrow R > V / I_{th} = 1.2 \cdot 10^5 \Omega$