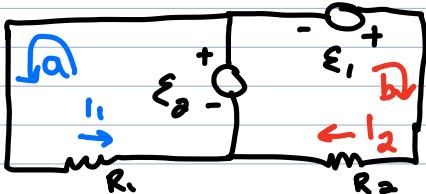


Exam 2 Thursday 5:00 in PS 239

Bring notes on one side of an 8½" x 11" sheet of paper

Optional review session Wednesday @ 7:00 pm in STEM 195




$$\begin{aligned}\epsilon_1 &= 10V & \epsilon_2 &= 20V \\ R_1 &= 10\Omega & R_2 &= 50\Omega\end{aligned}$$

loop rule for a: $\Delta V = 0 \Rightarrow \epsilon_2 - I_1 R_1 = 0 \Rightarrow I_1 = \frac{\epsilon_2}{R_1} = 2A$

loop rule for b: $\Delta V = 0 \Rightarrow \epsilon_1 - I_2 R_2 + \epsilon_2 = 0 \Rightarrow I_2 = \frac{\epsilon_1 + \epsilon_2}{R_2} = 0.6A$


Req in parallel situations

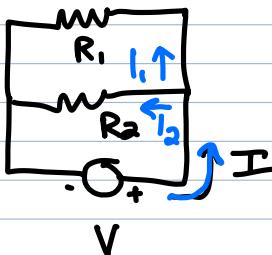

$$V = V_1 = V_2 \text{ and } I = I_1 + I_2 \Rightarrow \frac{V}{R_{\text{req}}} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow \frac{1}{R_{\text{req}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

If the four light bulbs are identical, which circuit puts out more light?

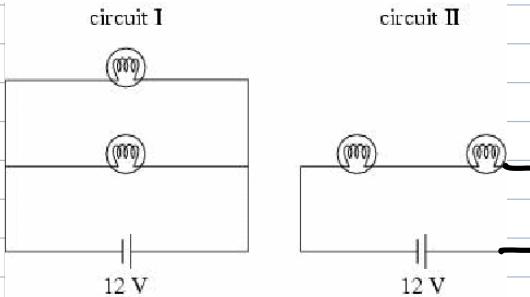
- a) I
- b) II
- c) They emit the same amount



Concept Q #2 ch 10


The circuit shows two identical bulbs glowing with equal brightness. When the switch is closed, the brightness of bulb A

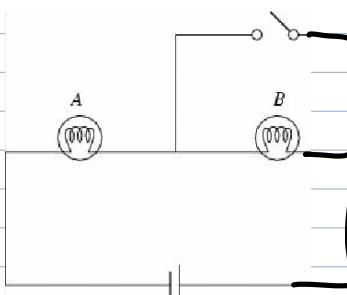- a) increases.
- b) decreases.
- c) remains the same.
- d) not enough information



Concept Q #3

example

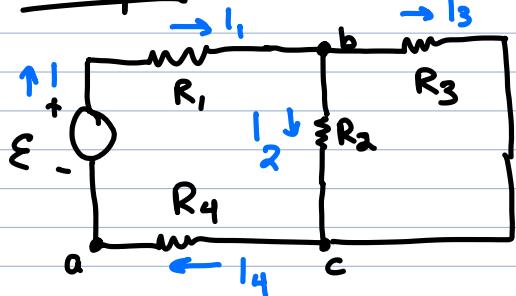


What is I through the battery?

$$\epsilon = 12V \quad R_1 = R_2 = 20\Omega \quad R_3 = 30\Omega \quad R_4 = 80\Omega$$

- Draw picture and label it

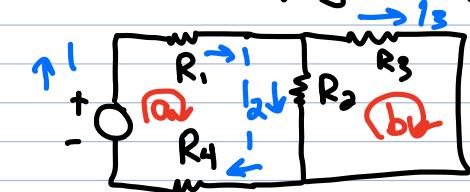- Use junction rule to eliminate extraneous subscripts on currents
- Pick a mini-circuit loop and apply $\sum V = 0$
- Continue looping through mini-circuits until all elements covered



$$a) \sum V = 0 : \epsilon - I R_1 - I_2 R_2 - I R_4 = 0$$

$$b) \sum V = 0 : -I_3 R_3 + I_2 R_2 = 0$$

$$c) \sum I = 0 \text{ at point } b : I = I_2 + I_3$$

$$a) \Rightarrow I_2 = \frac{\epsilon - I(R_1 + R_4)}{R_2}$$

3 equations, 3 unknowns ✓

$$b) I_3 = I_2 \frac{R_2}{R_3} = \frac{\epsilon - I(R_1 + R_4)}{R_2} \frac{R_2}{R_3} = \frac{\epsilon - I(R_1 + R_4)}{R_3}$$

$$c) I = \frac{\epsilon - I(R_1 + R_4)}{R_2} + \frac{\epsilon - I(R_1 + R_4)}{R_3} \Rightarrow I = \frac{\epsilon(R_2 + R_3)}{R_2 R_3 + (R_1 + R_4)(R_2 + R_3)} = 0.107A$$