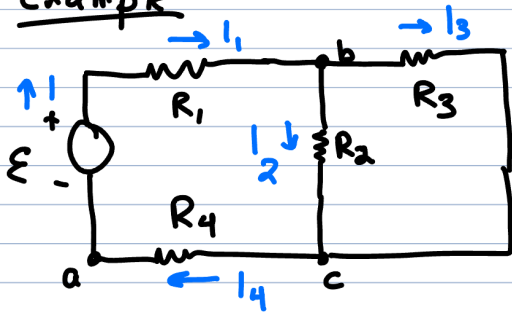


Circuit Lollapalooza

EXAMPLE




"RC" circuit from A1



An easier alternative: realize that R_2 & R_3 are in parallel
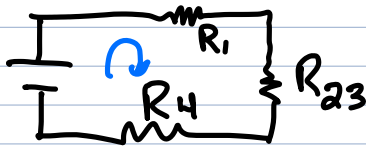
$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = 12 \Omega$$



$$\sum \Delta V = 0 : \epsilon - I(R_1 + R_{23} + R_4) = 0$$

$$\rightarrow I = \frac{\epsilon}{R_1 + R_{23} + R_4} = 0.107 \text{ A}$$

Conceptual follow-up: what should we expect for I if $R_2 \gg R_1, R_3, R_4$

$$\text{math: } R_{23} = \frac{R_2 R_3}{R_2 + R_3} \rightarrow R_3$$

inspection: current would ignore $R_2 \rightarrow I = \frac{\epsilon}{R_1 + R_3 + R_4}$

Q: Suppose you want to maximize the lifetime of the battery here, and to do so you may remove one resistor. If $R_1 = R_2 = R_3 = R_4$ which should you remove?

Brute force way:

To maximize the lifetime, minimize power output $P = \frac{\text{energy}}{\text{time}}$

and $P = \epsilon^2 / R_{eq} \Rightarrow$ thus maximize R_{eq}




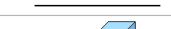
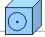
$$R_{eq} = R_1 + R_{23} + R_4 = \frac{5}{2} R$$

removing R_1 or R_4 : $R_{eq} = \frac{3}{2} R$
 removing R_2 or R_3 : $R_{eq} = \frac{6}{2} R$ } Remove R_2 or R_3


Pondering: resistors in parallel decrease overall R_{eq} , so remove one of them

It's 4:00 pm on October 31, and you just realized that it was your job to contribute the scary sound for this year's haunted house.



Supplies at hand:

-  resistor
-  capacitor
-  12 V battery
-  copper wire
-  speaker - 50 Hz and 70 db (scary!)


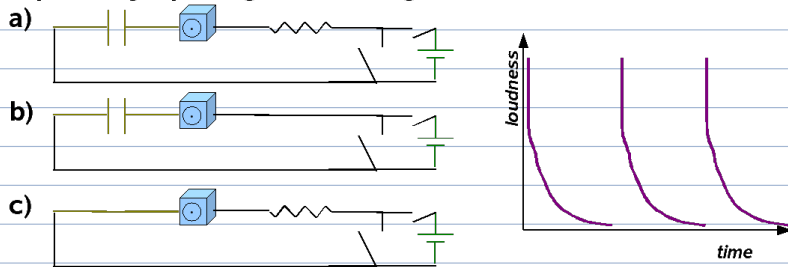
For optimal scariness, you should modulate the sound by repeatedly opening and closing:





option c

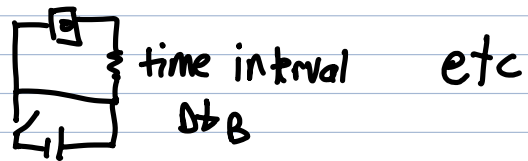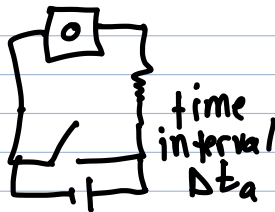

opening and closing switches gives

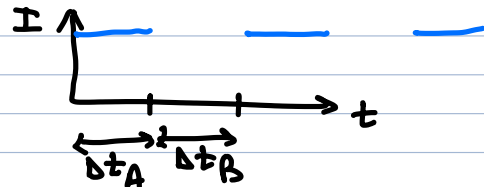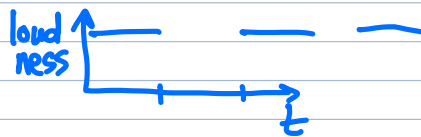


option b

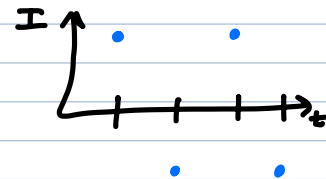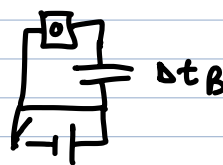

(assume speaker) instantaneous currents, has no r for charging & discharging



option a

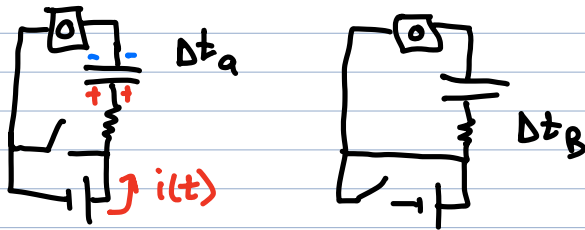

in Δt_A , charge builds up on capacitor $V_c(t) = q(t)/C$ ($\mathcal{E} \neq 0$)

until at some much later time t_f $V_c(t_f) \approx \frac{Q_f}{C}$

"loop it" : $\mathcal{E} - i(t)R - \frac{q(t)}{C} = 0$

$$i = \frac{dq}{dt} \Rightarrow \mathcal{E} - \frac{dq(t)}{dt}R - \frac{q(t)}{C} = 0$$

$q(t) = C\mathcal{E}(1 - e^{-t/RC})$ charging capacitor in RC circuit

Does this eqⁿ work?

$$q(0) = 0 \quad \checkmark$$


$$q(t_f \rightarrow \infty) = C\mathcal{E} \quad \checkmark$$

the current is $\frac{dq(t)}{dt} = C\mathcal{E}\left(0 + \frac{1}{RC}e^{-t/RC}\right) = \frac{\mathcal{E}}{R}e^{-t/RC}$


Does this work?

$$i(0) = \mathcal{E}/R \quad \checkmark$$
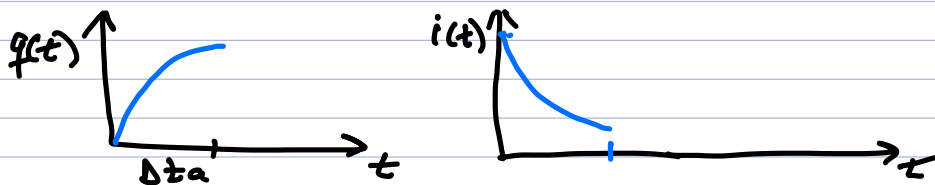
$$i(t_f \rightarrow \infty) = 0 \quad \checkmark$$



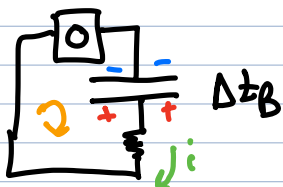in Δt_B what happens when the battery is removed?
capacitor discharges





"loop it" $-iR - \frac{q}{C} = 0 \Rightarrow i(t) = -\frac{q(t)}{RC}$

$$\Rightarrow \frac{dq(t)}{dt} = -\frac{q(t)}{RC} \Rightarrow \int_Q^q \frac{dq'}{q'} = \int_0^t -\frac{dt'}{RC}$$

$$\ln \frac{q}{Q} = \frac{-t}{RC} \Rightarrow q = Q e^{-t/RC}$$

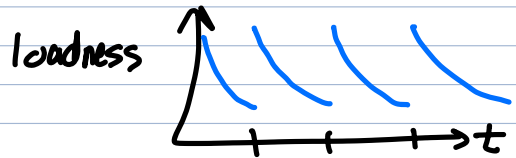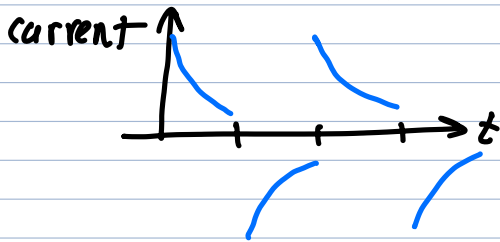
$$i = \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/RC}$$



This is a portion of a circuit loop.


- a) Current flows clockwise.
- b) Current flows counterclockwise.
- c) Current direction depends on the rest of the circuit.

ch 10 Concept Q #4

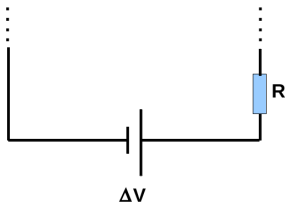

Why are batteries in a flashlight connected in series?

(assume no internal)

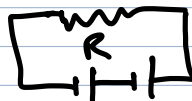

$$I = \frac{\mathcal{E}}{R}$$

Would there be any advantages to having them in parallel?



$$I = \frac{\mathcal{E}}{R} \quad \text{half the brightness}$$

\Rightarrow lasts longer

also, still works if one battery dies

concept Q #6 ch 10

same ΔV and twice the resistance? $\frac{1}{2}$ the current \rightarrow 1A

#7 c) light bulb gets short-circuited

#8