

## Continuing with chapter 8

### Super Wednesday bonus fun

How does the magnitude of the charge change, from Case a to Case b?

i) inserting dielectric causes induced polarization within  
→ ability to attract more charge

ii) compute  $Q = C \Delta V$

Case a potential difference across each capacitor is  $\Delta V/2$


$$Q = C_1 \Delta V_1 = C_2 \Delta V_2 = C_1 \frac{\Delta V}{2} = C_2 \frac{\Delta V}{2}$$

alternatively,  $\Delta V = \Delta V_1 + \Delta V_2$

imagine 2 sets of stairs:

$$\Delta V = \frac{Q}{C_1} + \frac{Q}{C_2} \Rightarrow \frac{\Delta V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_{eq}}$$

series

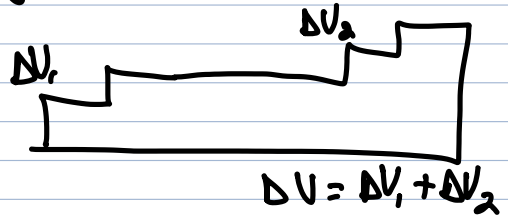


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \xrightarrow{C_1 = C_2 = C} \frac{C}{2}$$

Case b:  $C_{eq} = \frac{kC^2}{kC + C} = \frac{kC}{k+1} = \frac{C}{\frac{1}{k} + 1} > \frac{C}{2}$  since  $k > 1$


also:  $Q_{case b} = \frac{kC}{k+1} \Delta V > Q_{case a} = \frac{C}{2} \Delta V$

One capacitor, one battery:

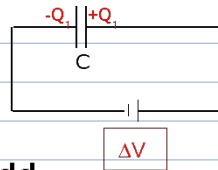


How are the various charges related if I add an exact copy of the capacitor in series?

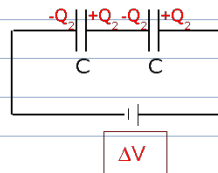- a)  $Q_1 = Q_2$
- b)  $Q_1 > Q_2$
- c)  $Q_1 < Q_2$
- d)  $Q_1 = \{Q_2 + 42\}^{1/2}$



$$C_{eq} = \frac{C}{2} \Rightarrow Q = \frac{C}{2} \Delta V$$

### Capacitors in parallel


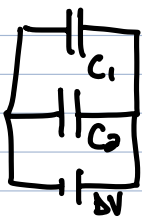


They have the same potential "drop"


We know  $\Delta V_1 = \Delta V_2 = \Delta V$   
 $Q_1/C_1 \quad Q_2/C_2 \quad Q_{tot}/C_{eq}$

also know  $Q_{tot} = Q_1 + Q_2 = C_1 \Delta V_1 + C_2 \Delta V_2 = C_1 \Delta V + C_2 \Delta V$   
 $\rightarrow C_1 + C_2 = Q/\Delta V = C_{eq}$   
 parallel


### Different capacitor combinations

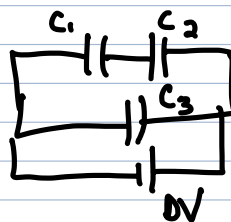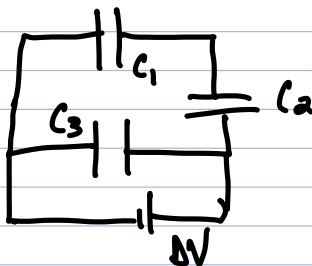


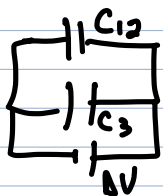
$C_1$  &  $C_2$  in series  
 $\rightarrow C_{12} = \frac{C_1 C_2}{C_1 + C_2}$



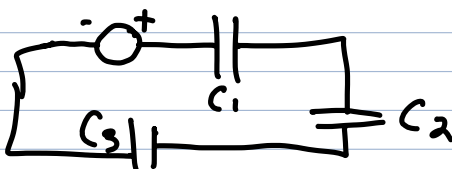
and  $C_{12}$  in parallel with  $C_3 \Rightarrow C_{123} = C_{12} + C_3$



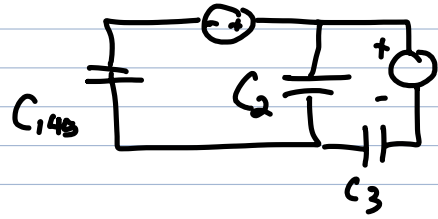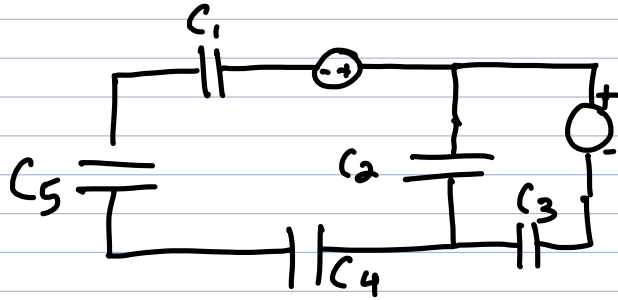
~~$C_{123} = C_1 + C_2 + C_3 = C_1 + C_2 + C_3$~~   
 ~~$= \frac{C_1 C_2 C_3}{C_1 + C_2 + C_3}$~~



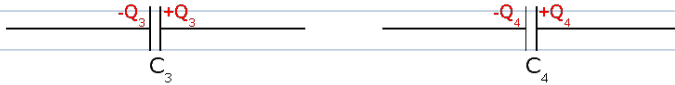Two capacitors are charged, but they are not connected:



Suppose I connect them:

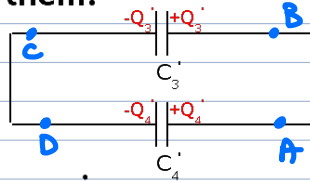

Concept Q #3

parallel b/c  $V_A - V_D = V_B - V_C$

The capacitors are now in

- a) series
- b) parallel ✓ awesome effort!

Q: What is  $V_B - V_C$ ?  $C_{eq} = C_3' + C_4' = C_3 + C_4$  (capacitances haven't changed)

$$Q_{total} = Q_3' + Q_4' = Q_3 + Q_4 \quad (\text{conservation of charge})$$

and since  $\frac{Q_{tot}}{C_{eq}} = \Delta V$  and  $\Delta V = V_B - V_C = V_A - V_D$

$$\implies V_B - V_C = \frac{Q_3 + Q_4}{C_3 + C_4}$$

Q: What are  $Q_3'$  and  $Q_4'$ ?

$$Q_3' = C_3' (V_B - V_C) = C_3 \left( \frac{Q_3 + Q_4}{C_3 + C_4} \right)$$

$$Q_4' = C_4' (V_A - V_D) = C_4 \left( \frac{Q_3 + Q_4}{C_3 + C_4} \right)$$

Numbers:  $C_3 = 2 \mu F$        $C_4 = 4 \mu F$   
 $Q_3 = 24 \mu C$        $Q_4 = 12 \mu C$   
 $V_3 = 12 V$        $V_4 = 3 V$

$$Q_3' = 2 \mu\text{F} \frac{36 \mu\text{C}}{6 \mu\text{F}}$$
$$= 12 \mu\text{C}$$

$$Q_4' = 4 \mu\text{F} \frac{36 \mu\text{C}}{6 \mu\text{F}}$$
$$= 24 \mu\text{C}$$

( $V_3' = 6\text{V}$  and  $V_4' = 6\text{V} \Rightarrow$  parallel)

Work on tutorial pp 94 (2<sup>nd</sup> half), 95, 96