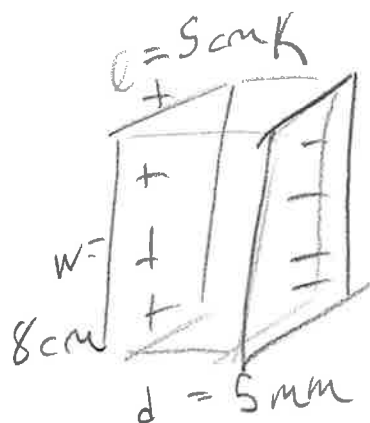


Warm up Problem

①



$$C = K \epsilon_0 \frac{A}{d}$$

$$A = l \cdot w$$

$$C = K \epsilon_0 \frac{lw}{d}$$

$$K = \frac{C d}{\epsilon_0 l w}$$

$$C \geq 34.7 \text{ pF}$$

$$K \geq 4.90$$


Bakelite, Neoprene rubber, pyrex glass,
Strontium titanate, water

$$C = \epsilon_0 \frac{A}{d}$$

②

$$C = 7.08 \text{ pF}$$

Circuits

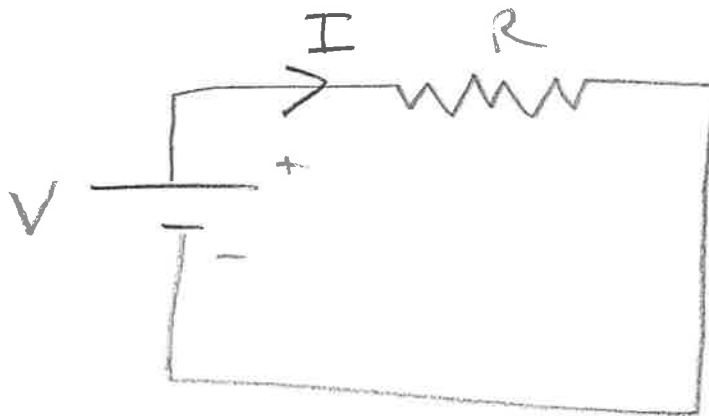

Symbols

$\begin{array}{c} + \\ \text{---} \\ \text{---} \end{array}$ - battery

--- - resistor

--- - wire

$\begin{array}{c} + \\ \text{---} \\ \text{---} \end{array}$ - capacitor

- current is the flow of positive charges.

Ohm's Law

③

$$V = IR$$

V - voltage (V)

I - current (Amps)

R - resistance (Ω Ohms)

$$1 \text{ A} = 1 \text{ C/s}$$

$$1 \Omega = 1 \text{ Js/C}^2$$

Ohm's Law Example

A 12V car battery delivers 2.5A through a vehicle's headlights. What is the resistance of the lights?

$$V = IR$$


$$R = \frac{V}{I}$$

$$\boxed{R = 4.8 \Omega}$$


Capacitors in Series and Parallel

(4)


Series

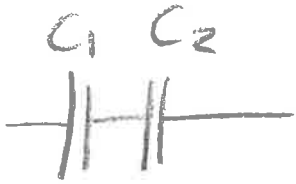

Parallel

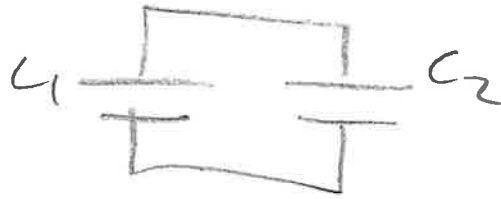

Series

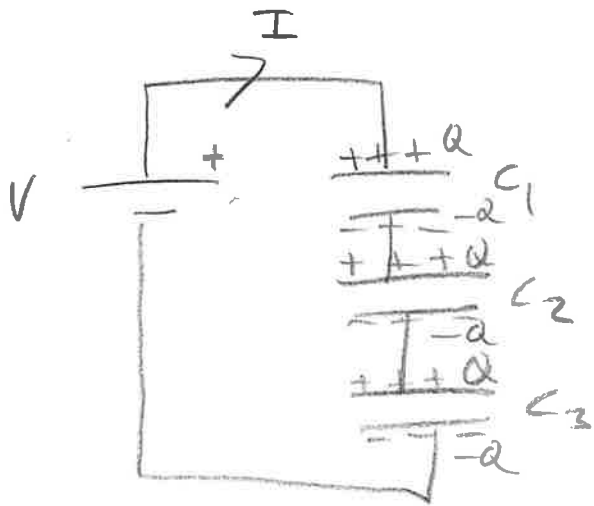

- capacitors have same charge (by conservation of charge).

simplifies to

$$V = V_1 + V_2 + V_3$$



$$V = V_s$$

$$V = \frac{Q}{C}$$

$$\frac{Q}{C_s} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\boxed{\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$$

5

Capacitors in series.

- equivalent capacitor is always smaller than smallest constituent capacitor.

Capacitors in series

Three capacitors ($1\mu\text{F}$, $5\mu\text{F}$, and $8\mu\text{F}$) are connected in series. Find the equivalent capacitance.


$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_s = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

$$\boxed{C_s = 0.755\mu\text{F}}$$

Capacitors in parallel

6

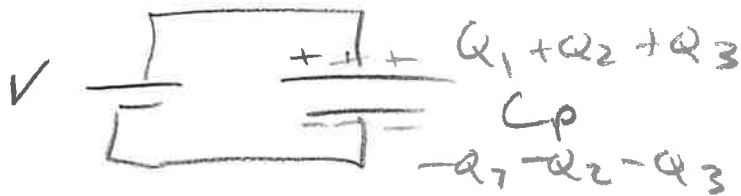


$$Q_1 + Q_2 + Q_3 = Q_p$$

$$C_1 V + C_2 V + C_3 V = C_p V$$

$$\boxed{C_p = C_1 + C_2 + C_3 + \dots}$$

Series and parallel example

Find the equivalent capacitance.

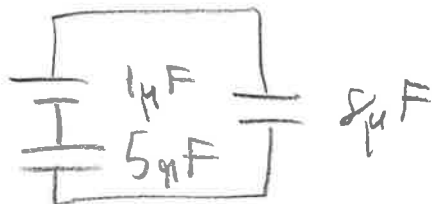

$$\frac{1}{C_{eq1}} = \frac{1}{5} + \frac{1}{1}$$

$$C_{eq1} = 0.833 \mu F$$

(7)



$$\frac{1}{T} C_{eq2}$$

$$C_{eq2} = C_{eq1} + 8 \mu F$$

$$C_{eq2} = 8.833 \mu F$$

Current


$$I = \frac{\Delta Q}{\Delta t}$$

I - current (Amps)


ΔQ - flow of charge (C)

Δt - rate of time (s)

$$1 A = 1 C/s$$

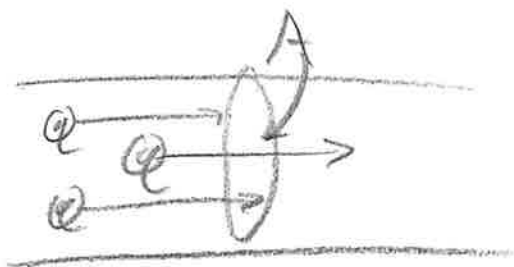


8

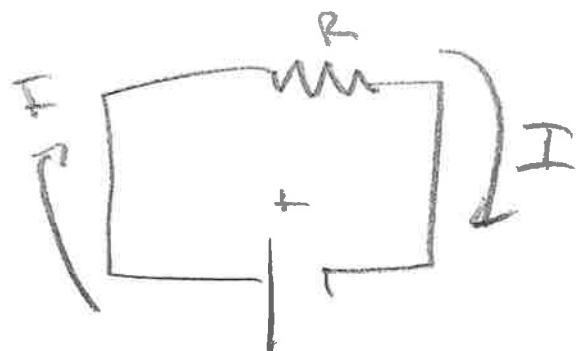

Drift velocity

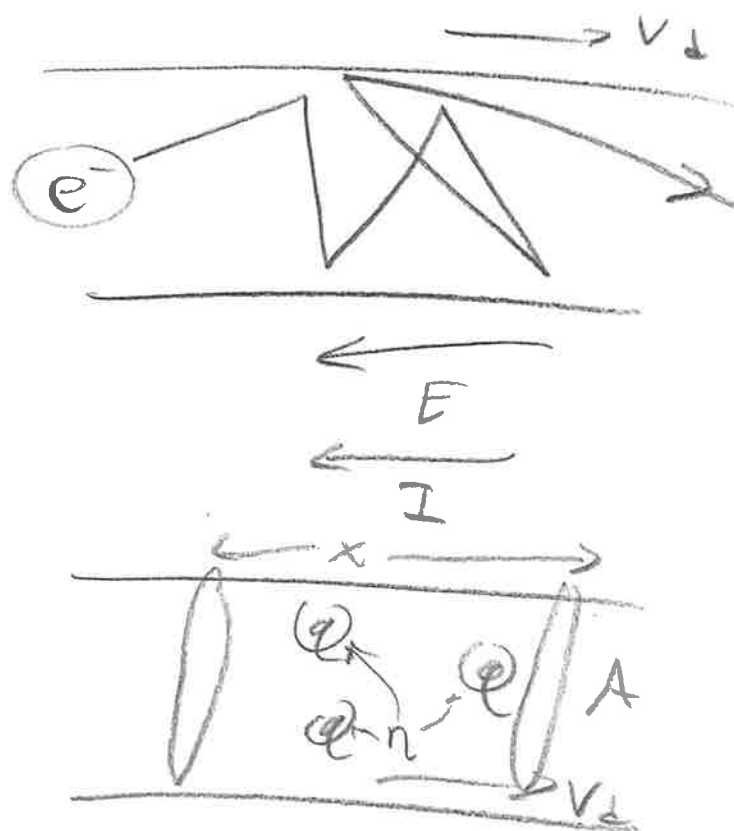— Flattening the motion of individual particles to the average, large-scale motion of free charges



n - free charges per volume

$$\frac{x}{t} = v_d$$

$$I = \frac{\Delta q}{\Delta t} = \frac{nqAx}{t}$$

$$\boxed{I = nqAv_d}$$

⑨

I - current (A)

n - free charges per unit volume ($/m^3$)


q - charge of particles (almost always $1.6 \times 10^{-19} C$)

A - cross-sectional area of wire (m^2)

v_d - drift velocity (m/s)

Drift velocity example

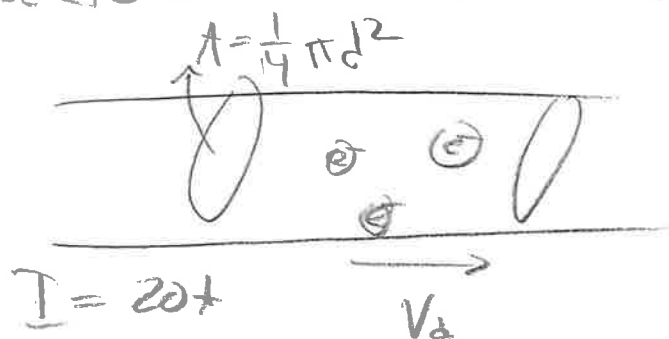Calculate the drift velocity of electrons in a copper wire with thickness $d = 2.053 mm$ carrying 20 A of current. There is $1e^-$ per Cu atom. The density of copper $8800 kg/m^3$ and has an atomic mass of 63.54 g/mol. Avogadro's number is $6.022 \times 10^{23} mol^{-1}$.



$$n = 1e^- / atom$$

$$d = 2.053 \times 10^{-3} m$$

$$q = -1.6 \times 10^{-19} C$$

(10)

$$I = nqAv_d$$

$$v_d = \frac{I}{nqA}$$

$$I = 20$$

$$A = \frac{1}{4} \pi d^2$$

$$n = 1 \cdot n_{Cu} = \frac{8800 \frac{\text{kg Cu}}{\text{m}^3}}{1 \text{ m}^3} \times \frac{1000 \text{ g Cu}}{1 \text{ kg Cu}}$$

$$\times \frac{1 \text{ mol Cu}}{63.54 \text{ g Cu}} \times \frac{6.022 \times 10^{23} \text{ atoms Cu}}{1 \text{ mol Cu}}$$

$$n = 8.34 \times 10^{28} \text{ e}^-/\text{m}^3$$

$$\ell = 1.6 \times 10^{-19}$$

$$V_d = 4.53 \times 10^{-4} \text{ m/s}$$