

RC Circuit Example

1. A 12 V battery is connected to a $2.5 \text{ M}\Omega$ resistor and $1 \text{ }\mu\text{F}$ capacitor.
 - a. Find $\tau = RC$.
 - b. Calculate the time to charge the capacitor to 75 % of its full charge.

