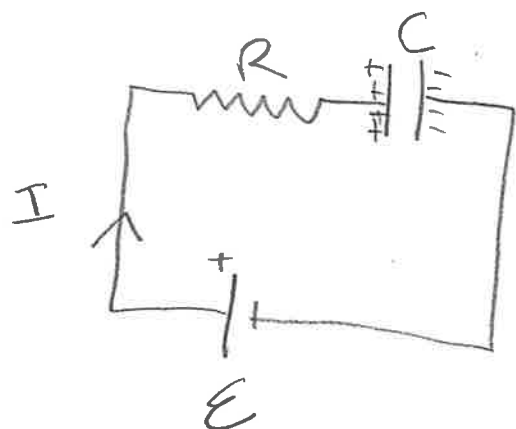


①

RC Circuit

Charging

— as charge builds on the capacitor, the current in the circuit decreases.

Use loop Rule!

$$\mathcal{E} - IR - V_C = 0$$

$$V_C = \frac{Q}{C}$$

$$\mathcal{E} - IR - \frac{Q}{C} = 0$$

— current in the circuit is the time derivative of charge on the capacitor.

$$I = \frac{dQ}{dt}$$

$$\mathcal{E} - \frac{dQ}{dt}R - \frac{Q}{C} = 0$$

Put Q terms on one side, t terms on the other. (2)

$$\mathcal{E} - \frac{dQ}{dt}R - \frac{Q}{C} = 0$$
$$+ \frac{dQ}{dt}R \quad + \frac{dQ}{dt}R$$

$$\mathcal{E} - \frac{Q}{C} = \frac{dQ}{dt}R$$

$$C\mathcal{E} - Q = \frac{dQ}{dt}RC$$

$$\frac{1}{RC} [C\mathcal{E} - Q] = \frac{dQ}{dt}$$

$$\frac{dQ}{C\mathcal{E} - Q} = \frac{dt}{RC}$$

First order, linear, differential equation

$$\int \frac{dQ}{C\mathcal{E} - Q} = \int \frac{dt}{RC}$$

$$u = C\mathcal{E} - Q$$

$$\frac{du}{dQ} = -1$$

$$du = -dQ$$

(3)

$$\int \frac{-du}{u} = \frac{1}{RC} \int dt$$

$$-\ln|u| + K = \frac{1}{RC}(t + K)$$

$$-\ln|CE - Q| + K = \frac{t}{RC} + K$$

$$-\ln|CE - Q| = \frac{t}{RC} + K$$

$$\ln|CE - Q| = -\frac{t}{RC} + K$$

$$CE - Q = e^{-t/RC + K}$$

$$CE - Q = e^{-t/RC} \cdot e^K$$

$$CE - Q = Ke^{-t/RC}$$

$$-Q = Ke^{-t/RC} - CE$$

$$Q = Ke^{-t/RC} + CE$$

Find K by plugging in initial conditions

$$Q(0) = 0$$

$$0 = Ke^0 + CE$$

$$0 = K + CE$$

$$K = -CE$$

$$Q(t) = CE \left[1 - e^{-t/RC} \right] \quad (4)$$

to solve for voltage, use $V = \frac{Q}{C}$

$$V(t) = \frac{Q(t)}{C}$$


$$V(t) = \frac{CE \left[1 - e^{-t/RC} \right]}{C}$$

$$V(t) = E \left[1 - e^{-t/RC} \right]$$

Define scale time $\tau = RC$ (RC has units seconds).

$$V(t) = E \left[1 - e^{-t/\tau} \right] \text{ (charging)}$$

Discharging case

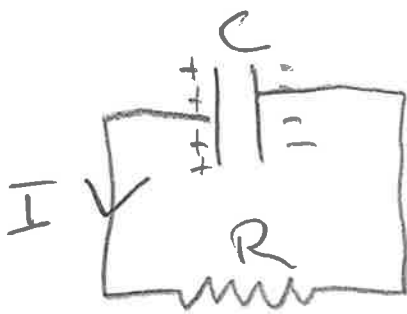

Loop Rule

$$V_C - IR = 0$$

- current in circuit is negative time-derivative of charge on capacitor. (5)

$$I = - \frac{dQ}{dt}$$

$$V_C - \frac{dQ}{dt} R = 0$$

$$\frac{Q}{C} + \frac{dQ}{dt} R = 0$$

Put Q terms on one side, t terms on other.

$$\frac{Q}{C} = - \frac{dQ}{dt} R$$

$$\frac{Q}{RC} = - \frac{dQ}{dt}$$

$$\int - \frac{dQ}{Q} = \int \frac{dt}{RC}$$

$$-\ln|Q| = \frac{t}{RC} + k$$

$$\ln|Q| = -\frac{t}{RC} + k$$

$$Q = e^{-t/RC + k}$$

$$Q = Ke^{-t/RC}$$

(6)

Plug in initial conditions

$$Q(0) = Q_{\max}$$

$$Q_{\max} = Ke^0$$

$$K = Q_{\max}$$

$$Q = Q_{\max} e^{-t/RC}$$

$$Q = CV$$

$$C V(t) = Q_{\max} e^{-t/RC}$$

$$V(t) = \frac{Q_{\max}}{C} e^{-t/RC}$$

$\frac{Q_{\max}}{C}$ is the voltage capacitor was charged to.


$$V(t) = \mathcal{E} e^{-t/RC}$$

$$RC = \tau$$

$$\boxed{V(t) = \mathcal{E} e^{-t/\tau} \text{ (discharging)}}$$

Charging

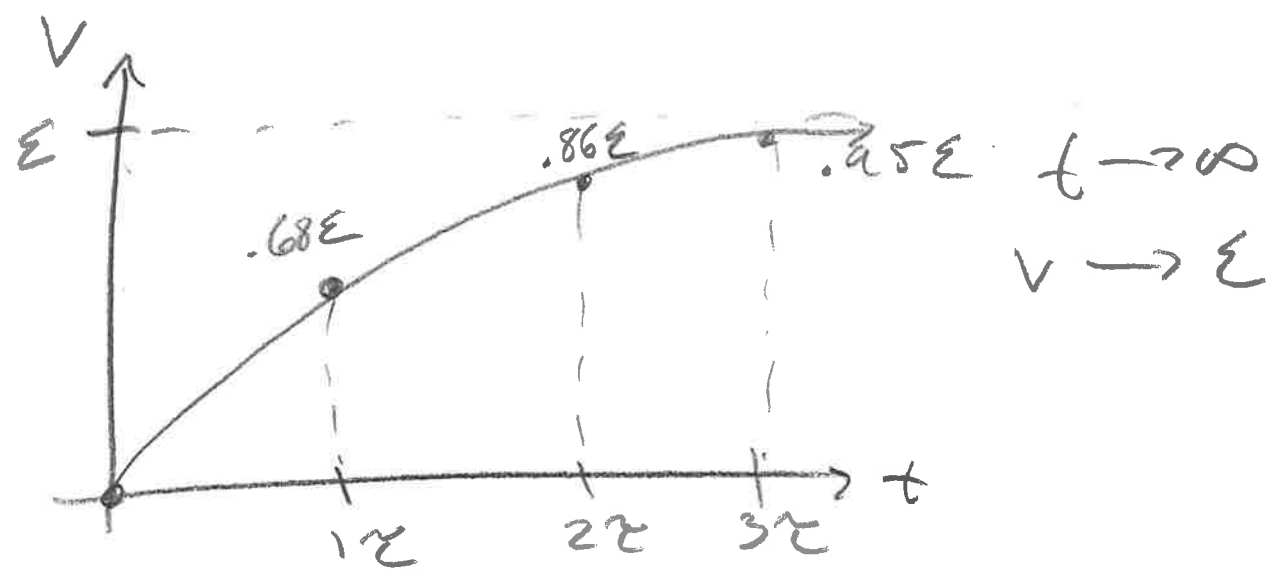
$$V = \mathcal{E} \left[1 - e^{-t/\tau} \right]$$



Discharging

$$V = \mathcal{E} e^{-t/\tau}$$

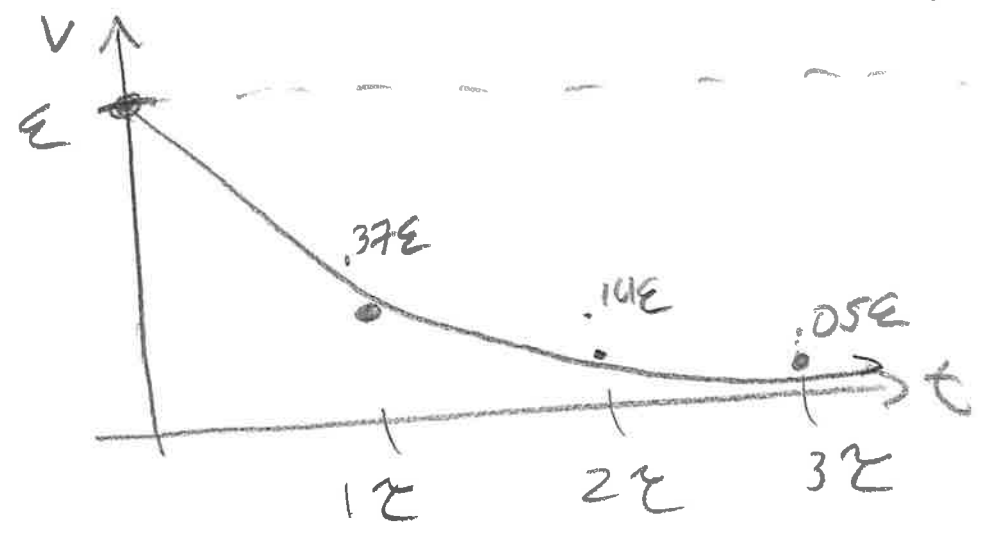$t \rightarrow \infty$
 $V \rightarrow 0$



Shape of curves dictated by
time constant $\tau = RC!$


⑧

RC Circuit Example

1. A 12V battery is connected to
2.5 M Ω resistor and a 1 μ F capacitor.

a) Find $\tau = RC$.

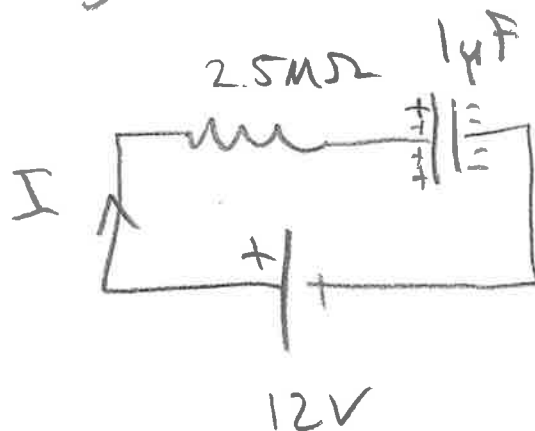b) Calculate the time to charge
the capacitor 75% its full
charge.



a) $\tau = RC$

$$\tau = (2.5 \times 10^6)(1 \times 10^{-6})$$

$$\boxed{\tau = 2.5 \text{ s}}$$

$$b) V(t) = 0.75 \mathcal{E}$$

$$t = ?$$

$$V(t) = \mathcal{E} \left[1 - e^{-t/\tau} \right]$$

$$\frac{V(t)}{\mathcal{E}} = 1 - e^{-t/\tau}$$

$$\frac{V(t)}{\mathcal{E}} - 1 = -e^{-t/\tau}$$

$$\ln | e^{-t/\tau} | = \ln \left| 1 - \frac{V(t)}{\mathcal{E}} \right|$$

$$-\frac{t}{\tau} = \ln \left| 1 - \frac{V(t)}{\mathcal{E}} \right|$$

$$t = -\tau \ln \left| 1 - \frac{V(t)}{\mathcal{E}} \right|$$

$$V(t) = 0.75 \mathcal{E}$$

$$\tau = 2.55$$

$$t = -2.55 \ln | 1 - 0.75 |$$

$$\boxed{t = 3.475}$$

$\tau < t < 2\tau$ as expected.

