
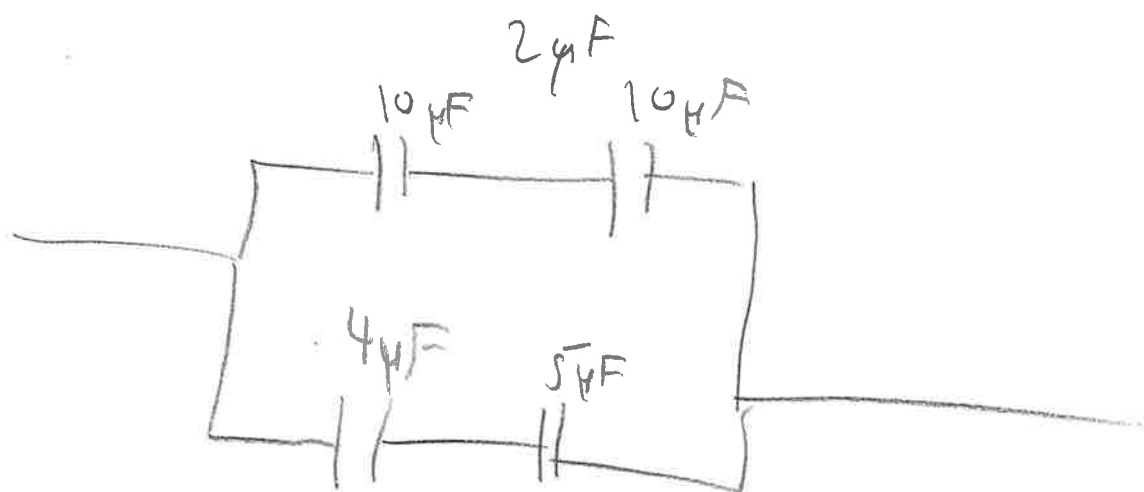


Warm up problem

①

$$C_{eq1} = C_1 + C_2$$

$$C_{eq1} = 10\mu F$$

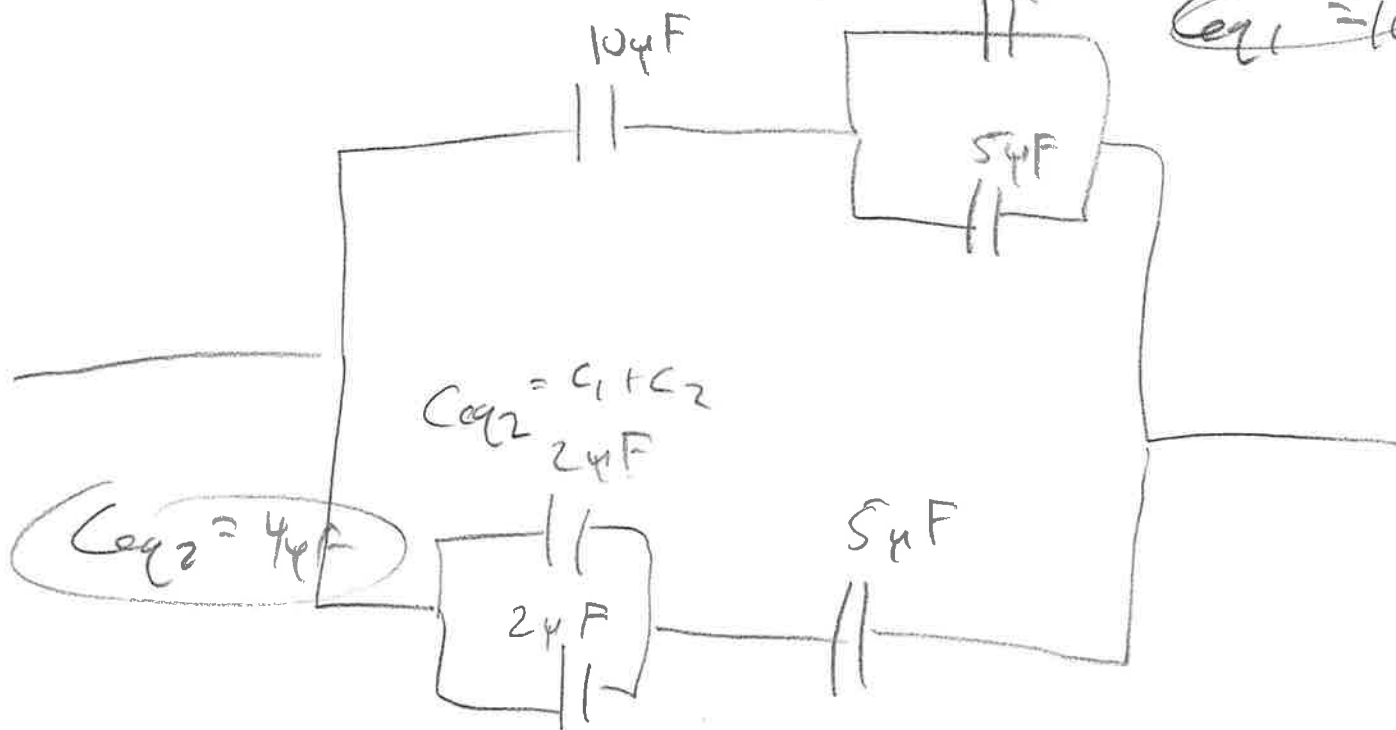

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$

$$C_{eq3} = \left(\frac{1}{10} + \frac{1}{10} \right)^{-1}$$

$$C_{eq3} = \left(\frac{2}{10} \right)^{-1}$$

$$C_{eq3} = 5 \mu F$$


$$C_{eq4} = \left(\frac{1}{4} + \frac{1}{5} \right)^{-1}$$

$$C_{eq4} = \left(\frac{5}{20} + \frac{4}{20} \right)^{-1}$$

$$C_{eq4} = \left(\frac{9}{20} \right)^{-1}$$

$$C_{eq4} = \frac{20}{9}$$

$$C_{eq4} = 2.22 \mu F$$

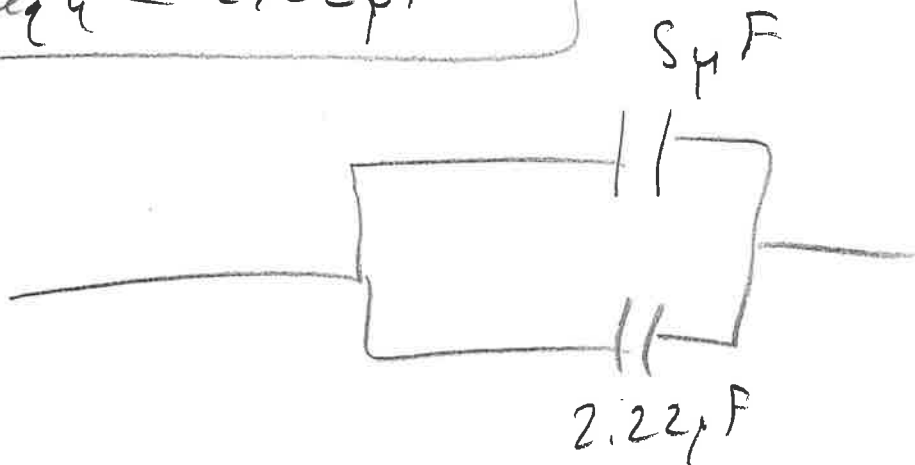


$$C_{eq\ total} = C_1 + C_2$$

(3)



$$C_{eq\text{total}} = 7.22 \mu\text{F}$$

Resistivity

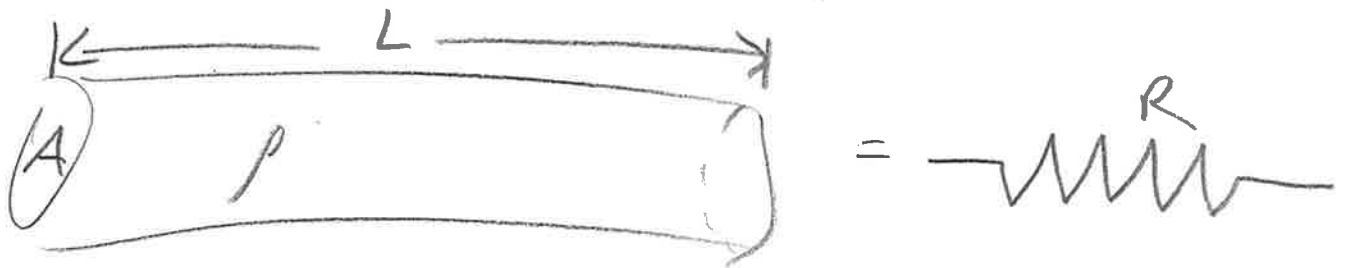

$$R = \rho \frac{L}{A}$$

R - resistance (Ω)

ρ - resistivity ($\Omega \cdot \text{m}$)

L - length of wire (m)

A - cross-sectional area (m^2)

ρ is property of the material.

Resistance Problem

what length of copper wire,
with diameter 1mm, is required
to produce 0.1 Ω of resistance? ④

$$R = \frac{\rho L}{A}$$

$$A = \frac{1}{4} \pi d^2$$

$$R = \frac{\rho L}{\frac{1}{4} \pi d^2}$$

$$R = \frac{4\rho L}{\pi d^2}$$

$$L = \frac{\pi d^2 R}{4}$$

$$\boxed{L = 4.57 \mu}$$

Resistors in Series

⑤



- $\Delta V_R = IR$ (Ohm's Law)

- current I is the same in series

$$IR_1 + IR_2 + IR_3 = IR_s$$


$$I(R_1 + R_2 + R_3) = I(R_s)$$

$$\boxed{R_s = R_1 + R_2 + R_3 + \dots}$$

Resistors add in series

Resistors in Parallel

(6)

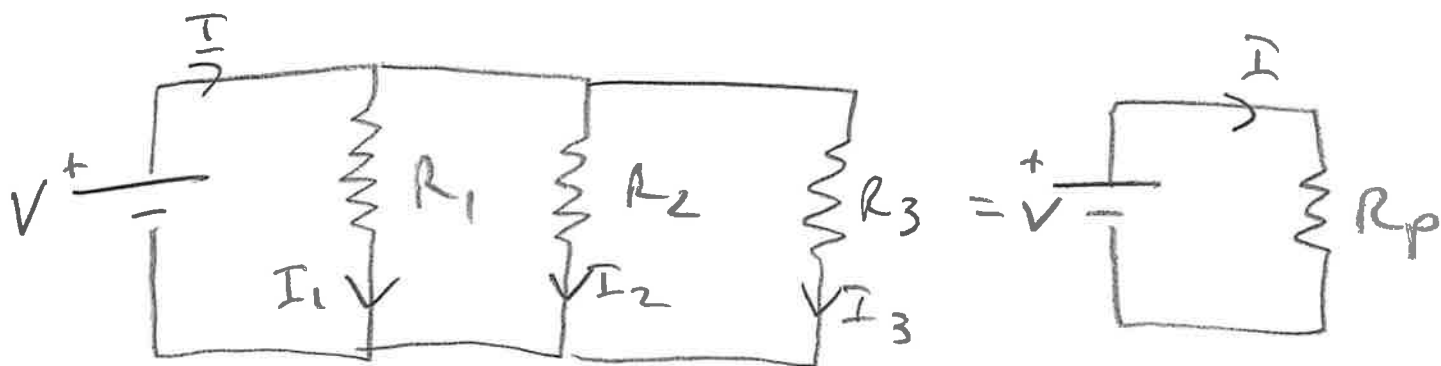

$$I = I_1 + I_2 + I_3$$

$$I_1 = \frac{V}{R_1} \quad \text{— voltage is the same in parallel.}$$


$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$V \left(\frac{1}{R_p} \right) = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\boxed{\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

Equivalent resistance in parallel is always less than the smallest constituent resistor.



7

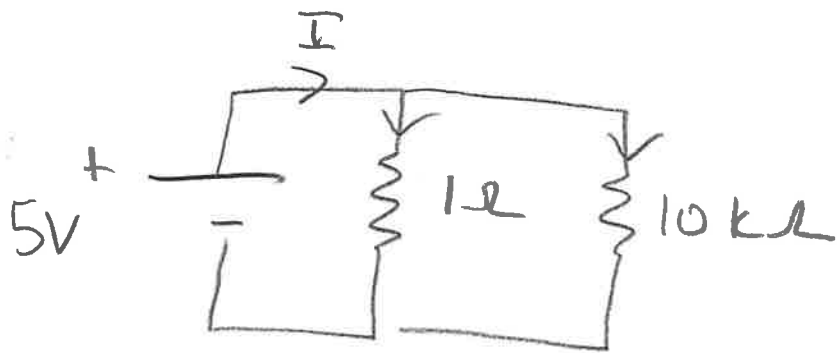


- Some current flows through the large resistor!

Equivalent Resistance Problem

Find the equivalent resistance.

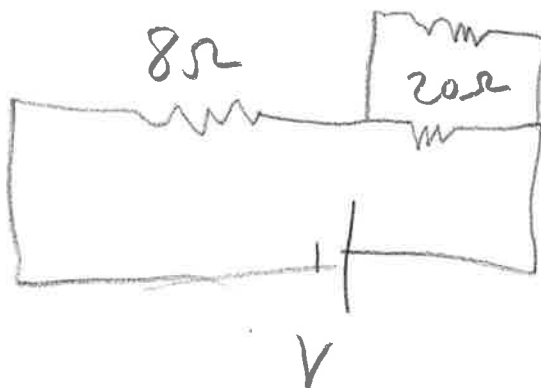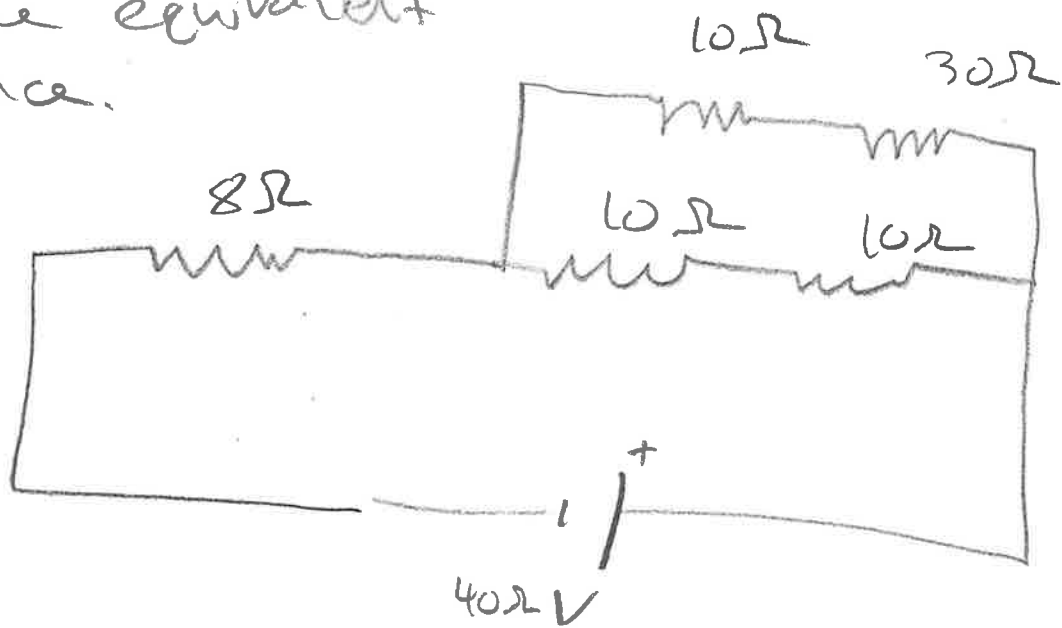

8

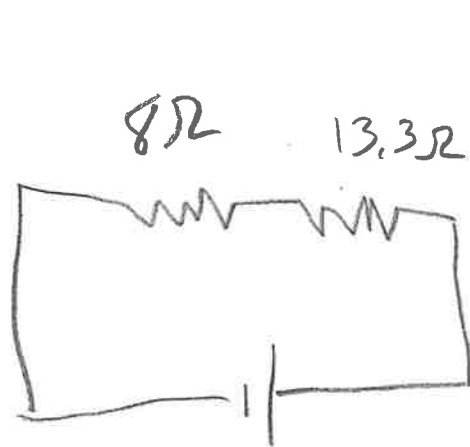

$$R_{eq} = \left(\frac{1}{20} + \frac{1}{40} \right)^{-1}$$

$$R_{eq} = \left(\frac{2}{40} + \frac{1}{40} \right)^{-1}$$

$$R_{eq} = \left(\frac{3}{40} \right)^{-1}$$

$$R_{eq} = \frac{40}{3}$$

$$R_{eq} = 13.3\Omega$$



$$R_{eq} = 21.3\Omega$$