

PHYS1120
Summer 2025

1. Find the equivalent capacitance for the circuit below.

