

Kirchoff's Rules

1. Find the current through each resistor.

