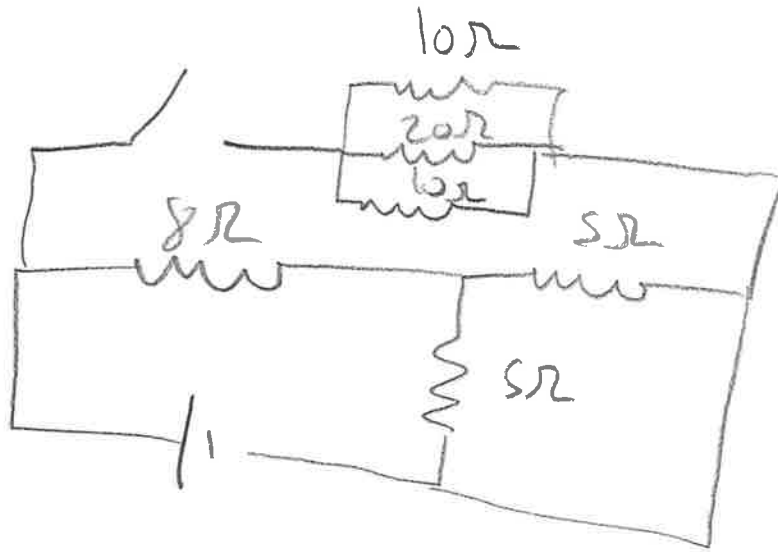



Warm Up Problem

①



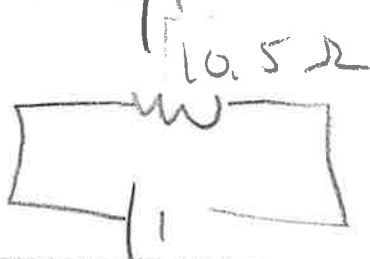a) Find the equivalent resistance when switch is open.

No current flows in top branch, circuit simplifies.



$R_{eq} = 10.5 \Omega$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{5}$$

$$\frac{1}{R_{eq}} = \frac{2}{5}$$


$$R_{eq} = \frac{5}{2} = 2.5$$

$$R_{eq} = 8 + 2.5$$

$$R_{eq} = 10.5$$

b) Now switch is closed. Current flows through all branches.


(2)

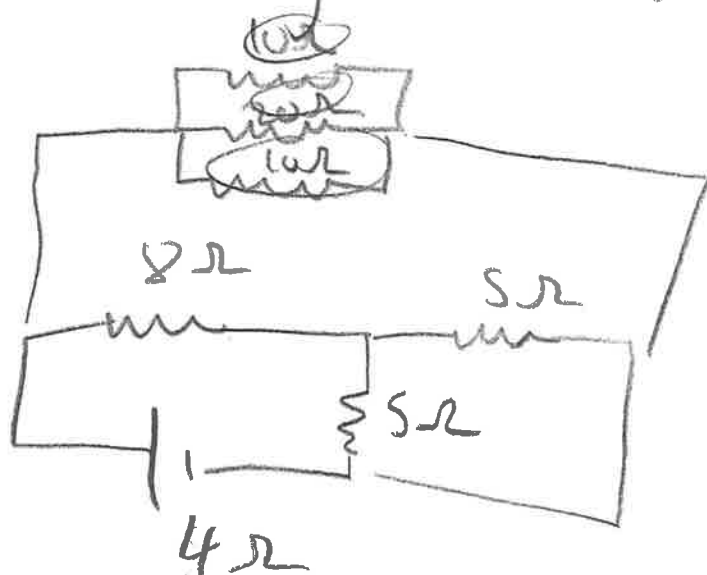

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{10}$$

$$\frac{1}{R_{eq}} = \frac{5}{20}$$


$$R_{eq} = 4\Omega$$

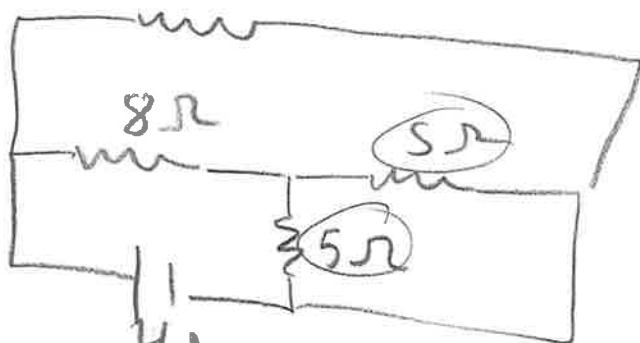

$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{5}$$

$$\frac{1}{R_{eq}} = \frac{2}{5}$$

$$R_{eq} = 2.5$$

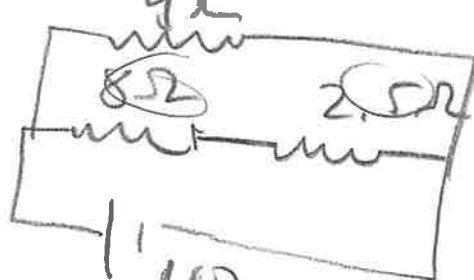

$$R_{eq} = R_1 + R_2$$


$$R_{eq} = 8 + 2.5$$

$$R_{eq} = 10.5$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{8} + \frac{2}{21}$$

$$\frac{1}{R_{eq}} = \frac{21 + 8}{84}$$

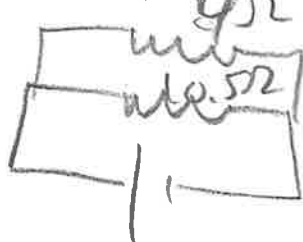


$$\frac{1}{R_{eq}} = \frac{29}{84}$$

③

$$R_{eq} = \frac{84}{29} = 2.897 \Omega$$


2.897 Ω

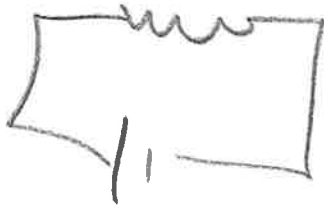

$$R_{eq} = 2.897 \Omega$$

Electromotive force

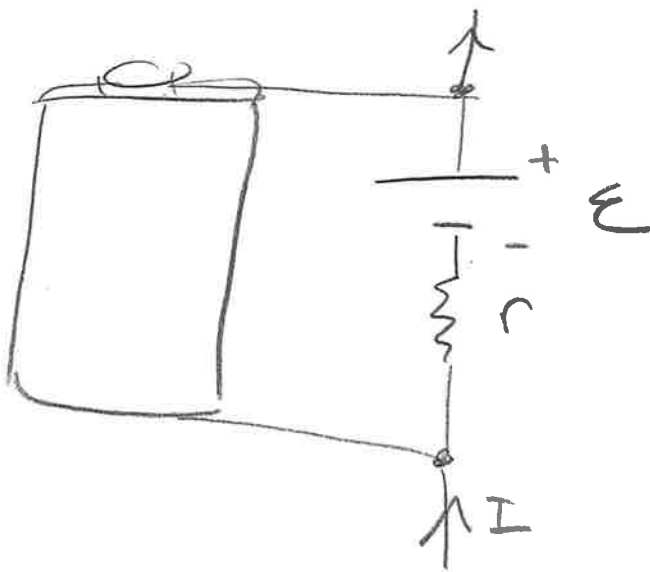- Potential difference of a voltage source when no current is flowing.



$$V = \mathcal{E} - Ir$$

V - terminal voltage (V)


$\mathcal{E}$ - electromotive force (emf).

I - current from battery (A)

r - internal resistance of battery (Ω)

Circuit with load

(4)

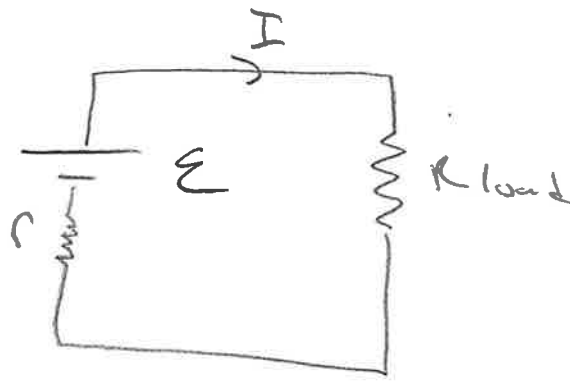

$$I = \frac{\mathcal{E}}{r + R_{load}}$$

r increases as battery is depleted


$\rightarrow$ less I for constant R_{load} .

Kirchoff's Rules

1. Junction Rule - the sum of all the currents entering a junction equals the sum of all the currents leaving the junction.
2. Loop Rule - the sum of all of the changes in voltage around any closed loop in a circuit is zero.

Junction Rule

⑤

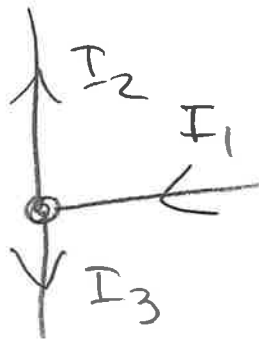


$$I_1 = I_2 + I_3$$

- for unknown circuit, direction is arbitrary.

↳ Assuming the wrong direction will give a negative current. When reporting your answer, flip assumed direction for all negative currents.

Loop Rule

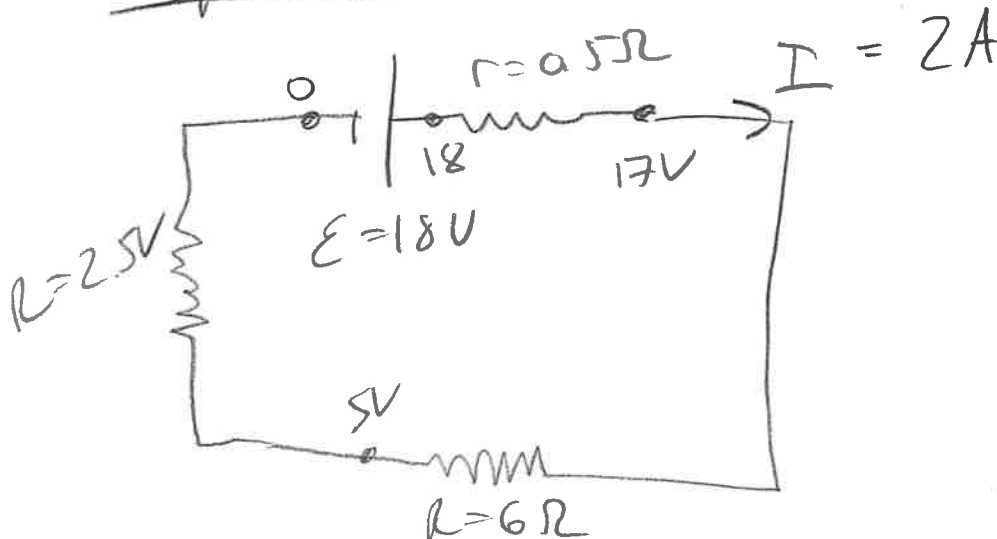


- Going from - to + on battery is positive V
- Going with current through a resistor is a drop.
- clockwise

Kirchoff's Rule Example

6.

Find the currents through all resistors.

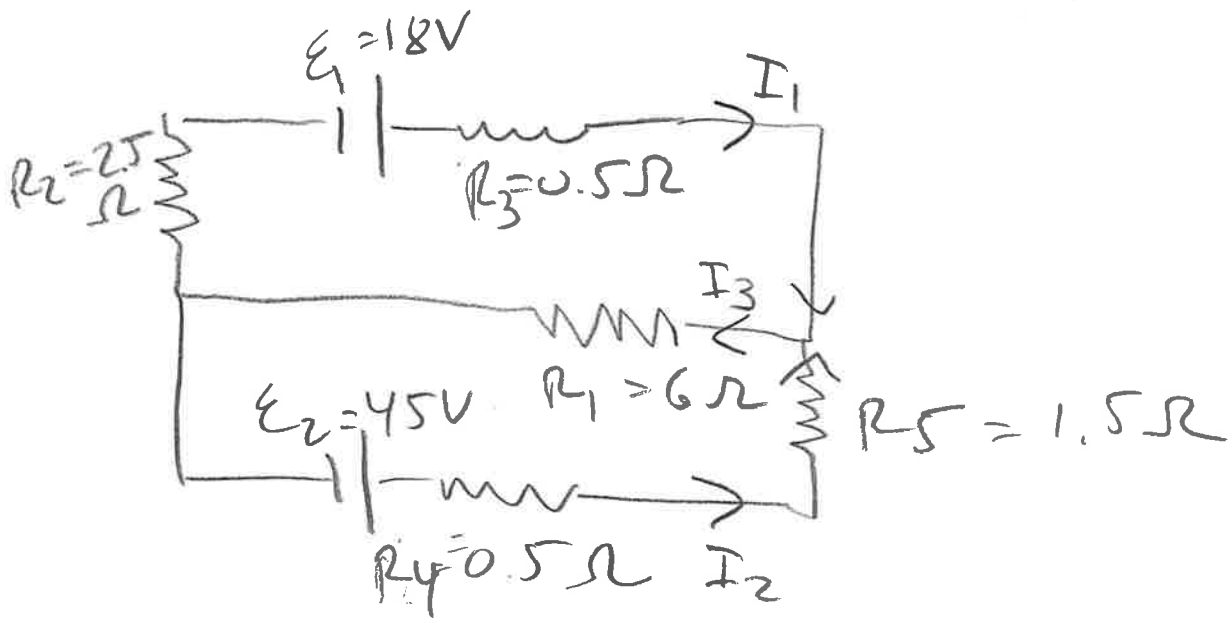

3 unknown currents

3 equations required

$$\textcircled{1} \quad 18 = 0.5 I_1 - 6 I_3 - 2.5 I_1 = 0$$

$$\textcircled{2} \quad 6 I_3 + 1.5 I_2 + 0.5 I_2 - 45 = 0$$

$$\textcircled{3} \quad I_1 + I_2 = I_3 \quad \text{Rewrite}$$

$$\textcircled{1} \quad -3 I_1 - 6 I_3 = -18$$

$$\textcircled{2} \quad 2 I_2 + 6 I_3 = 45$$

$$\textcircled{3} \quad I_1 + I_2 = I_3$$

Plug ③ into ① and ②

⑦

$$\textcircled{1} -3I_1 -6(I_1 + I_2) = -18$$

$$\textcircled{2} 2I_2 + 6(I_1 + I_2) = 45$$

$$\textcircled{1} -\underline{3I_1} -\underline{6I_1} + \cancel{6I_2} = -18$$

$$\textcircled{1} -9I_1 -\cancel{6I_2} = -18$$

$$\textcircled{2} \underline{2I_2} + \underline{6I_1} + \underline{6I_2} = 45$$

$$\textcircled{2} 6I_1 + 8I_2 = 45$$

use ② to solve for I_2 , plug into ①

$$6I_1 + 8I_2 = 45$$

$$8I_2 = 45 - 6I_1$$

$$I_2 = \frac{45}{8} - \frac{3}{4}I_1$$

$$\textcircled{1} -9I_1 -6I_2 = -18$$

$$-9I_1 -6\left[\frac{45}{8} - \frac{3}{4}I_1\right] = -18$$

$$-9I_1 -\frac{3 \cdot 45}{4} + \frac{18}{4}I_1 = -18$$

$$I_1 \left[-9 + \frac{9}{2} \right] + \frac{135}{4} = -18 \quad (8)$$

$$I_1 \left(-\frac{9}{2} \right) = \frac{-72 + 135}{4}$$

$$I_1 \left(-\frac{9}{2} \right) = \frac{63}{4}$$

$$I_1 = \frac{63}{2 \cdot 9} \cdot + \frac{2}{9}$$

$$I_1 = \frac{63}{2 \cdot 9}$$

$$I_1 = \frac{7}{2}$$

$$I_1 = 3.5 \text{ A}$$

From before

$$I_2 = \frac{45}{8} - \frac{3}{4} I_1$$

$$I_2 = \frac{45}{8} - \frac{3}{4} \left(-\frac{7}{2} \right)$$

$$I_2 = \frac{45}{8} + \frac{21}{8}$$

$$I_2 = \frac{66}{8}$$

9

$$I_2 = \frac{33}{4}$$

$$I_2 = 8.25 A$$


$$I_3 = I_1 + I_2$$

$$I_3 = -\frac{7}{2} + \frac{33}{4}$$

$$I_3 = \frac{33 - 14}{4}$$

$$I_3 = \frac{19}{4}$$

$$I_3 = 4.75 A$$

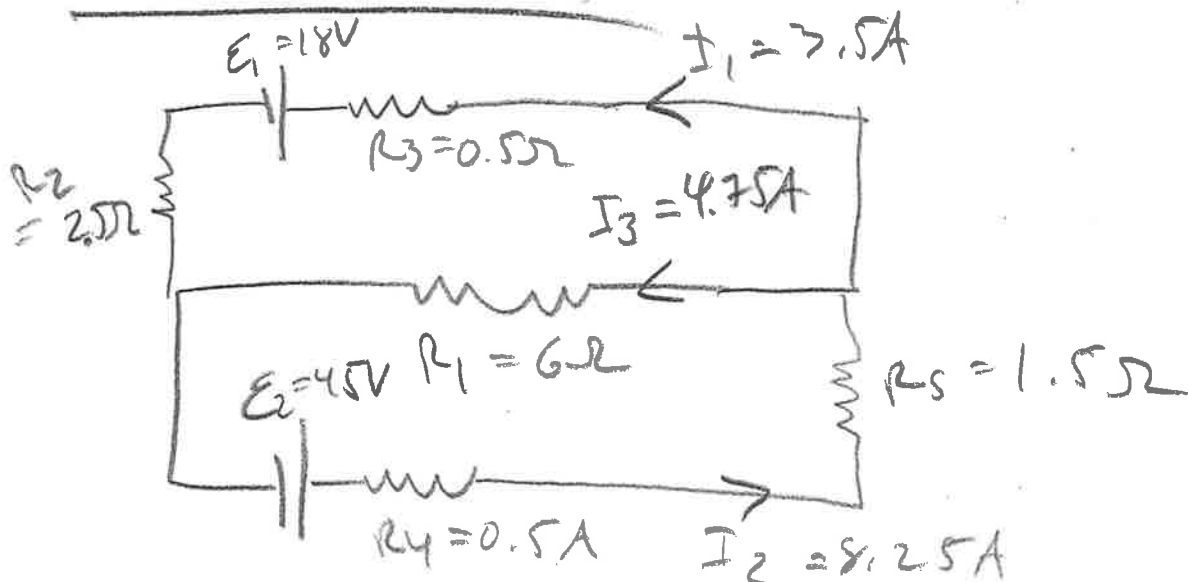

Use row reduction

(10)

$$\textcircled{1} \quad -3I_1 + 0I_2 - 6I_3 = -18$$

$$0I_1 + 2I_2 + 6I_3 = 45$$

$$1I_1 + 1I_2 - 1I_3 = 0$$

$$\begin{array}{c} I_1 \quad I_2 \quad I_3 \\ \left[\begin{array}{ccc|c} -3 & 0 & -6 & -18 \\ 0 & 2 & 6 & 45 \\ 1 & 1 & -1 & 0 \end{array} \right] \end{array}$$

↓

$$\begin{array}{c} I_1 \quad I_2 \quad I_3 \\ \left[\begin{array}{ccc|c} 1 & 0 & 0 & -3.5 \\ 0 & 1 & 0 & 8.25 \\ 0 & 0 & 1 & 4.75 \end{array} \right] \end{array}$$

$$\begin{aligned} I_1 &= -3.5A \\ I_2 &= 8.25A \\ I_3 &= 4.75 \end{aligned}$$

Same
answer!

Voltmeter

①

- voltage is the same in parallel
- connect voltmeters in parallel

Ammeter

- current is the same in series,
- connect ammeter in series.

