

PHYS1120  
Summer 2025

---

1. A circuit is shown below.

- (a) Find the equivalent resistance when the switch is open.
- (b) Now find the equivalent resistance after the switch is closed.

