

Chapter 30: Inductance

- Mutual Inductance
- Self Inductance
- R-L, L-C, R-L-C circuits


Mutual Inductance

$$\epsilon_1 = -N_1 \frac{d\Phi_{B1}}{dt} \quad \epsilon_2 = -N_2 \frac{d\Phi_{B2}}{dt}$$

$$\Phi_{B2} = \oint \vec{B}_1 \cdot d\vec{A}$$

$$N_2 \Phi_{B2} = M_{21} I_1$$
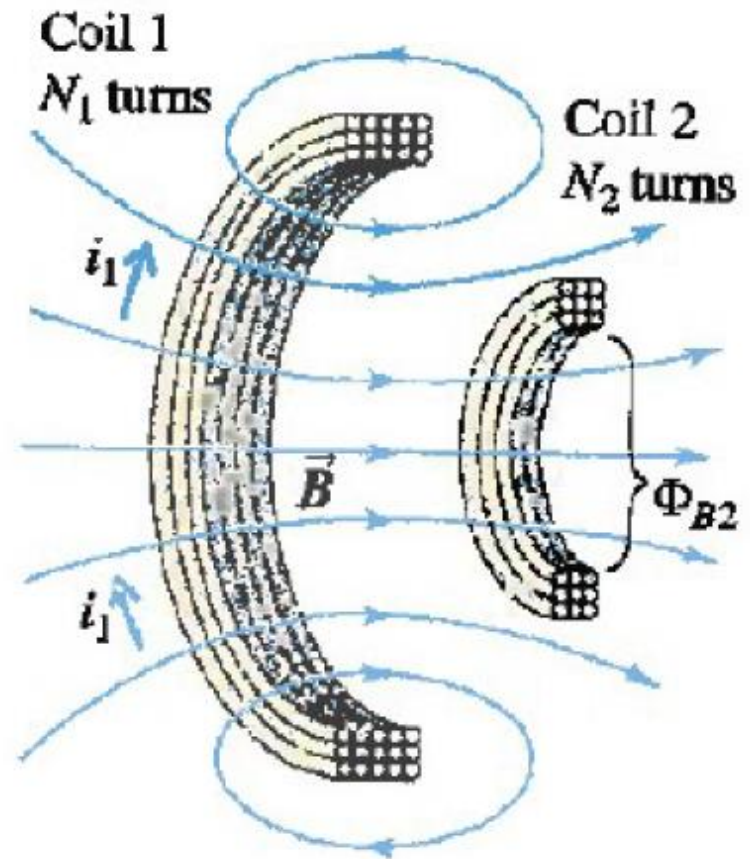
$$\epsilon_1 = -M \frac{dI_2}{dt} \quad \epsilon_2 = -M \frac{dI_1}{dt}$$



Unit for the mutual inductance: henry (H)

$$1 \text{ H} = 1 \text{ Wb/A} = 1 \text{ V}\cdot\text{s/A} = 1 \text{ }\Omega\cdot\text{s} = 1 \text{ J/A}^2$$


Example

In one form of Tesla coil (a high-voltage generator popular in science museums), a long solenoid with length l and cross-sectional area A is closely wound with N_1 turns of wire. A coil with N_2 turns surrounds it at its center. Find the mutual inductance M .

Self Inductance

$$L = \frac{N \Phi_B}{I}$$
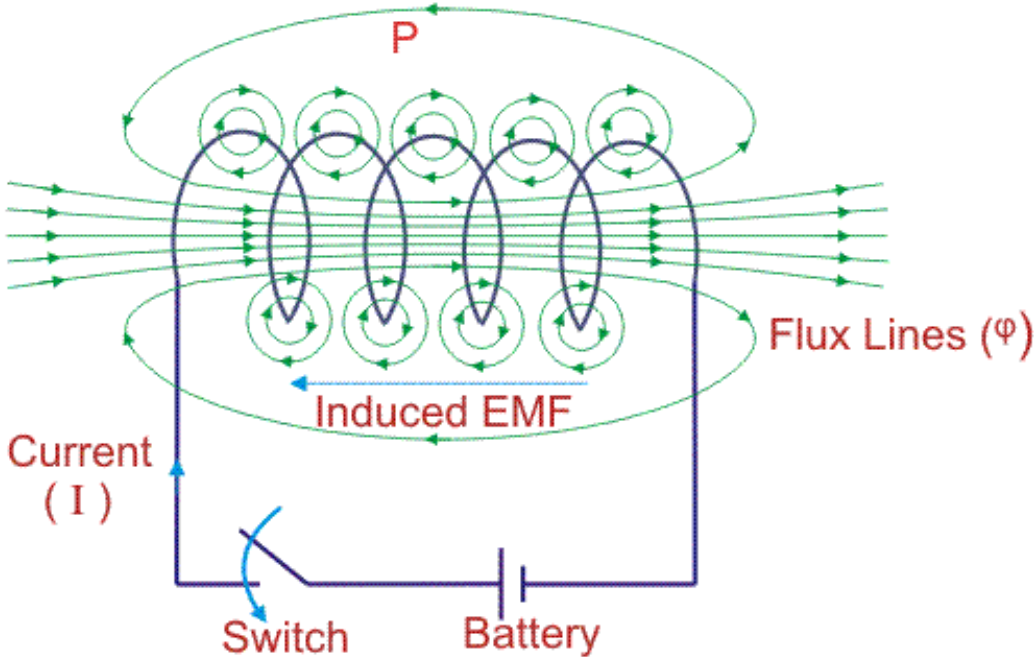
$$\epsilon = -N \frac{d \Phi_B}{dt} = -L \frac{dI}{dt}$$




R-L circuit

$$I(t) = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$

$$I(t) = I_0 e^{-(R/L)t}$$


Time constant: $\tau = \frac{L}{R}$

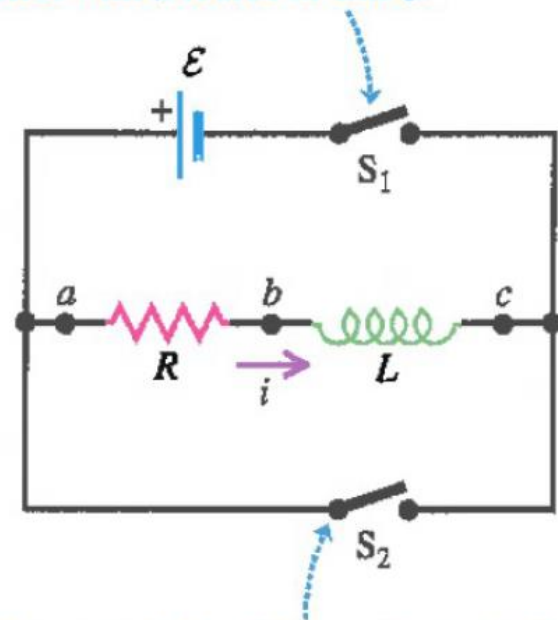Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .



Closing switch S_2 while opening switch S_1 disconnects the combination from the source.

L-C circuit

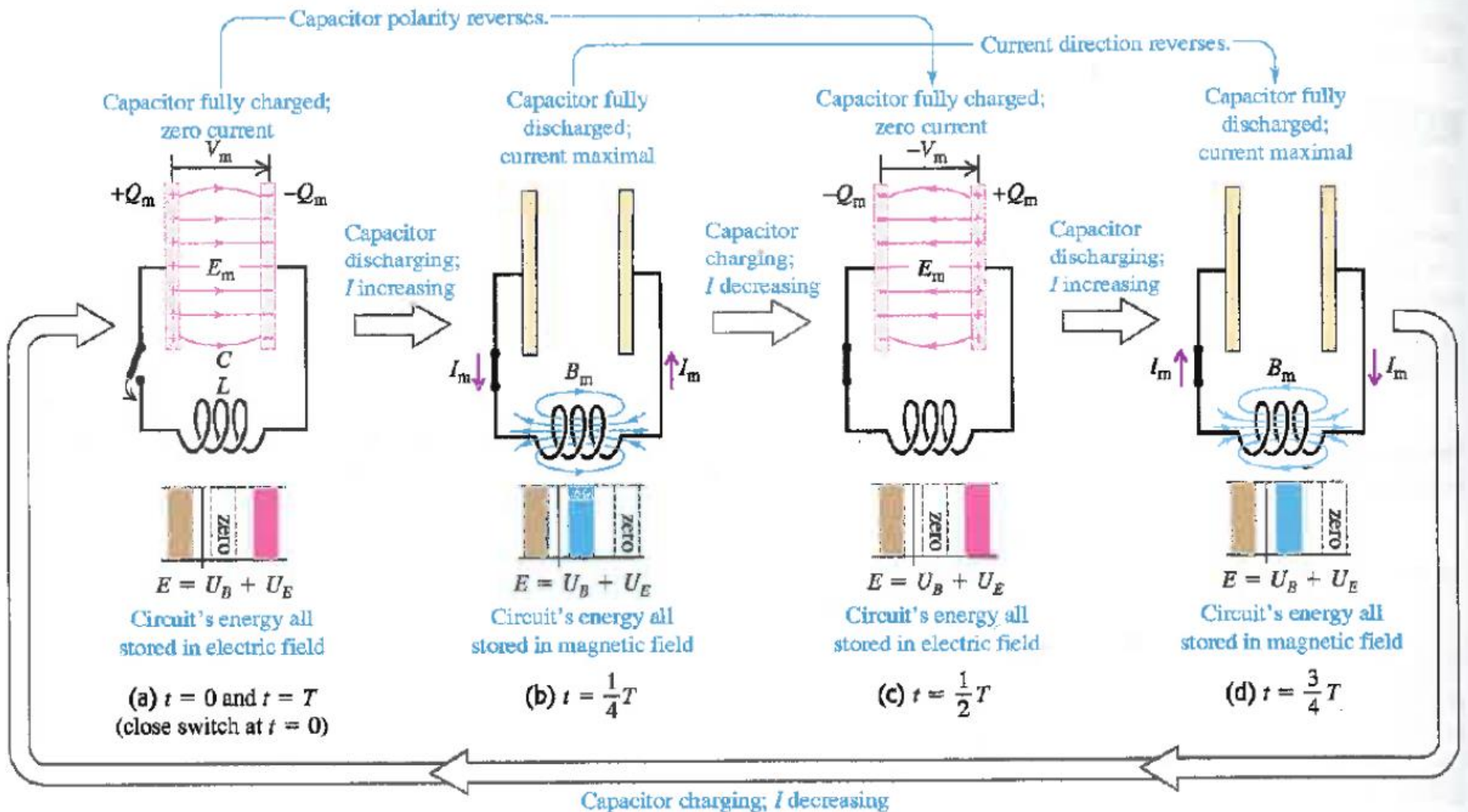

L-C circuit

$$q(t) = Q \cos(\omega t + \phi)$$

$$I(t) = -\omega Q \sin(\omega t + \phi)$$

$$\omega = 2\pi f = \sqrt{\frac{1}{LC}}$$

R-L-C circuit

$$q(t) = A e^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} t + \phi\right)$$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

